

CHAPTER 8

Combinational Circuit design and Simulation Using Gate

This chapter in the book includes:

- Objectives
- Study Guide
- 8.1 Review of Combinational Circuit Design
- 8.2 Design of Circuits with Limited Gate Fan-in
- 8.3 Gate delays and Timing Diagrams
- 8.4 Hazards in Combinational Logic
- 8.5 Simulation and Testing of Logic Circuits
- Problems
- Design Problems

Objectives

Topics introduced in this chapter:

- Draw a timing diagram for a combinational circuit with gate delays.
- Define **static 0-and 1-hazards and dynamic hazard**. Given a combinational circuit, find all of the static 0-and 1-hazards. For each hazard, specify the order in which the gate outputs must switch in order for the hazard to actually produce a false output.
- Given switching function, realize it using a two-level circuit which is **free of static and dynamic hazards** (for single input variable changes).
- Design a multiple-output NAND or NOR circuit using gates with limited fan-in.
- Explain the operation of a logic simulator that uses **four-valued logic**.
- Test and debug a logic circuit design using a simulator.

8.2 Design of Circuits with Limited Gate Fan-in

Example: Realize $f(a,b,c,d) = \sum m(0,3,4,5,8,9,10,14,15)$ using 3-input NOR gate

map of f :

$cd \backslash ab$	00	01	11	10
00	1	1	0	1
01	0	1	0	1
11	1	0	1	0
10	0	0	1	1


$$f' = a'b'c'd + ab'cd + abc' + a'bc + a'cd'$$

8.2 Design of Circuits with Limited Gate Fan-in

$$f' = b'd(a'c' + ac) + a'c(b + d') + abc'$$

$$f = [b + d' + (a + c)(a' + c')][a + c' + b'd][a' + b' + c]$$

Resulting NOR-gate of f

 

8.2 Design of Circuits with Limited Gate Fan-in

Example: Realize the functions given in Figure 8-2,
using only 2-input NAND gates and inverters.

If we minimize each function separately, the result is

 


Figure 8-2

Result

$$f_1 = b'c' + ab' + a'b$$

$$f_2 = b'c' + bc + a'b$$

$$f_3 = a'b'c + ab + bc'$$

8.2 Design of Circuits with Limited Gate Fan-in

$$f_1 = b'(a + c') + a'b$$

$$f_2 = (b'+c)(b+c') + a'b \quad (\text{or} \quad f_2 = b(a'+c) + b'c')$$

$$f_3 = a'b'c + b(a+c')$$

eliminate the remaining 3-input gate by Eq. $a'b'c = a'(b'c) = a'(b+c)'$


 
 


Figure 8-3: Realization of Figure 8-2



8.3 Gate Delays and Timing Diagrams

Propagation Delay in an Inverter

 



8.3 Gate Delays and Timing Diagrams

Timing Diagram for AND-NOR Circuit

  


8.3 Gate Delays and Timing Diagrams

Timing Diagram for Circuit with Delay

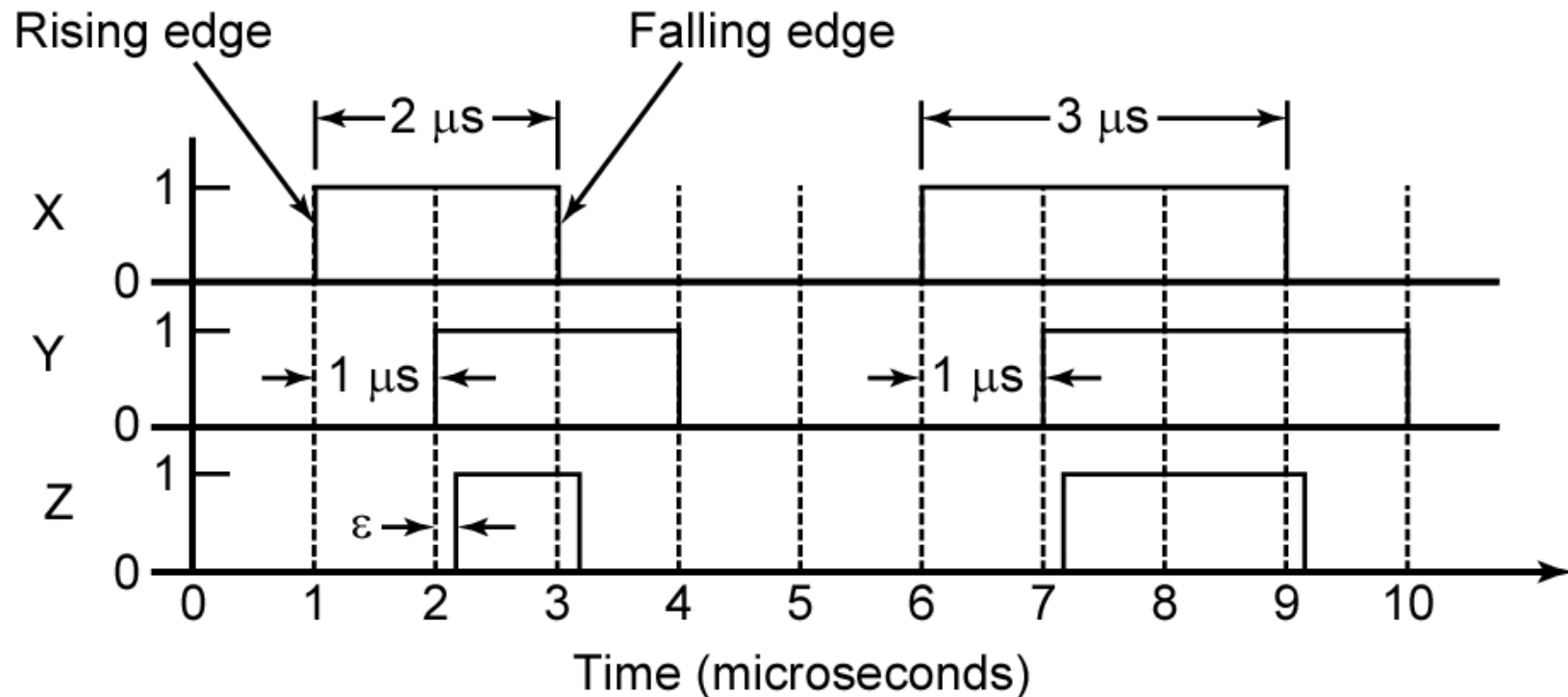 


8.4 Hazards in Combinational Logic


Types of Hazards

 

(a) Static 1-hazard

 


(b) Static 0-hazard

 


(c) Dynamic hazards

8.4 Hazards in Combinational Logic

Detection of a 1-Hazard

 


(a) Circuit with a static 1-hazard

 

(b) Timing chart

8.4 Hazards in Combinational Logic

Circuit with Hazard Removed

 

		A	
		0	1
BC	00	0	1
	01	0	1
	11	1	1
	10	0	0

8.4 Hazards in Combinational Logic

Detection of a Static 0-Hazard


$$F = (A + C)(A' + D')(B' + C' + D)$$

A=0, B=1,


D=0

Inverter 3ns
delay


Other Gates
5ns delay

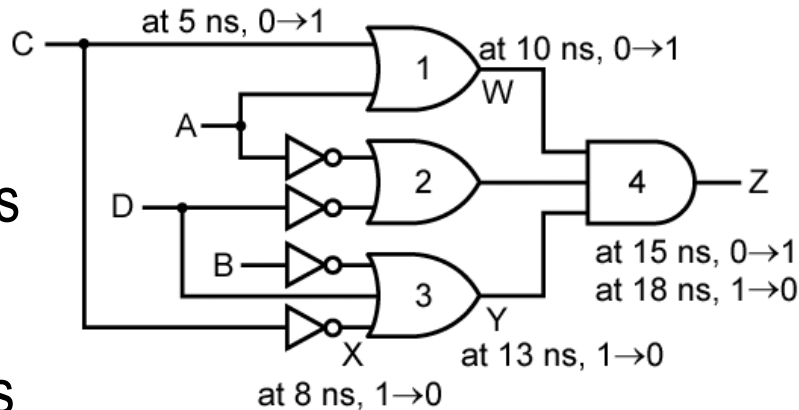

(a) Circuit with a static 0-hazard

 


(b) Karnaugh map for circuit of (a)

 

(c) Timing diagram illustrating 0-hazard of (a)



8.4 Hazards in Combinational Logic

Karnaugh Map Removing Hazards

 

$$F = (A + C)(A' + D')(B' + C' + D)(C + D')(A + B' + D)(A' + B' + C')$$

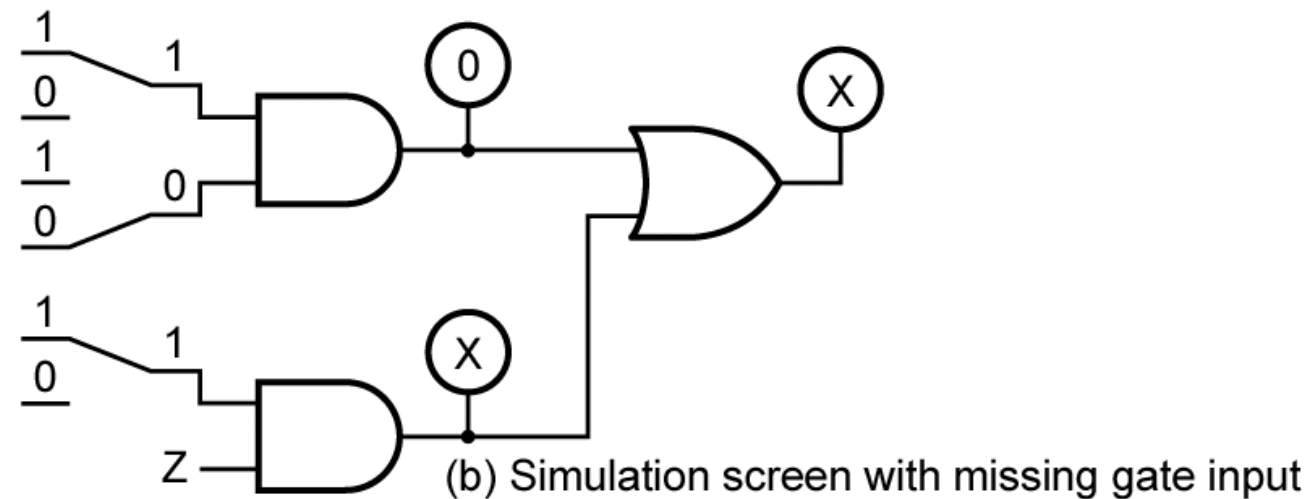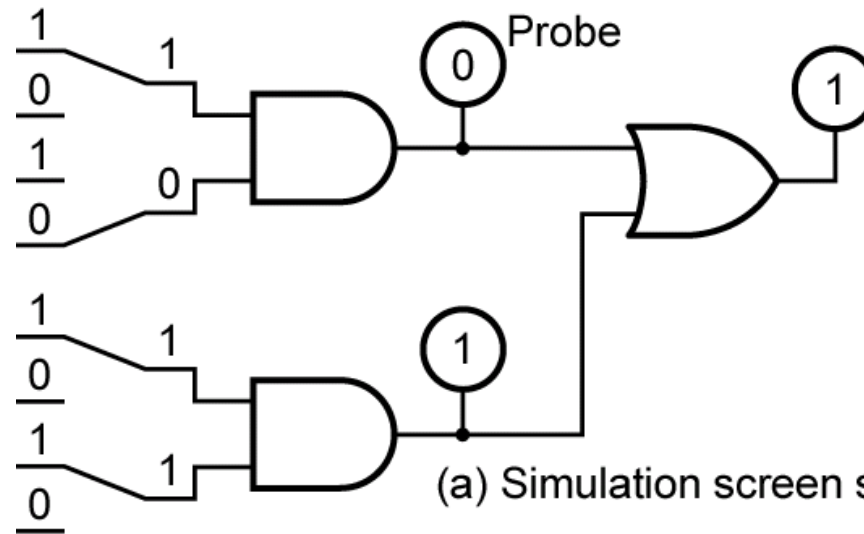8.5 Simulation and Testing of Logic Circuit



8.5 Simulation and Testing of Logic Circuit

And and OR Functions for Four-Valued Simulation

•	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X

+	0	1	X	Z
0	0	1	X	X
1	1	1	1	1
X	X	1	X	X
Z	X	1	X	X

8.5 Simulation and Testing of Logic Circuit

Logic Circuit with Incorrect Output

Example: $F = AB(C'D + CD') + A'B'(C + D)$

