

---

# Chapter 5

## Handy Circuit Analysis Techniques

- 5.1 Linearity and Superposition
- 5.2 Source Transformation
- 5.3 Thévenin and Norton Equivalent Circuits
- 5.4 Maximum Power Transfer
- 5.5 Delta–Wye Conversion
- 5.6 Selecting an Approach: A Summary of Various Techniques

- Linear Elements and Linear Circuits

**linear element:** a passive element that has a linear voltage-current relationship


**linear dependent source:** a dependent source whose output is proportional only to the first power of a specified variable in the circuit (or to the sum of such quantities)

$$v_s = 0.5i_1 + 3v_2 \quad \text{vs.} \quad v_s = 0.5i_1^2$$


**linear circuit:** a circuit composed entirely of independent sources, linear dependent sources, and linear elements.

- Superposition Theorem

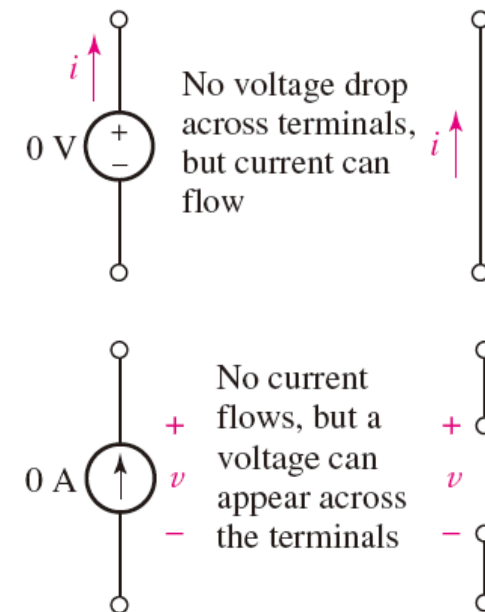In any linear resistive network, the voltage across or the current through any resistor or source may be calculated by **adding algebraically all the individual voltages or currents** caused by **the separate independent sources acting alone**, with all other independent sources "turned off" or "zeroed out".




## 5.1 Linearity and Superposition

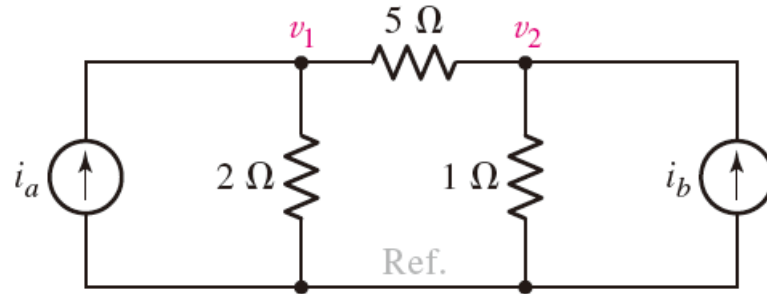

$$\text{Node 1: } i_a = \frac{v_1}{2} + \frac{v_1 - v_2}{5} = 0.7v_1 - 0.2v_2$$

$$\text{Node 2: } i_b = \frac{v_2}{1} + \frac{v_2 - v_1}{5} = -0.2v_1 + 1.2v_2$$

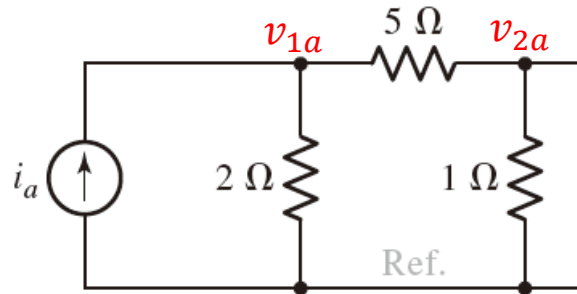
$$\Rightarrow v_1 = 1.5i_a + 0.25i_b, \quad v_2 = 0.25i_a + 0.875i_b$$



$$\text{Node 1: } i_a = \frac{v_1}{2} + \frac{v_1 - v_2}{5} = 0.7v_1 - 0.2v_2$$

$$\text{Node 2: } \frac{v_2}{1} = \frac{v_1 - v_2}{5} \rightarrow 0.2v_1 - 1.2v_2 = 0$$
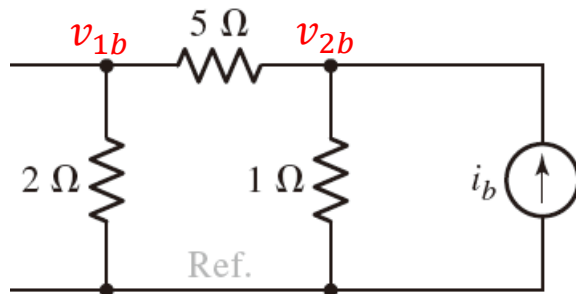
$$\Rightarrow v_{1a} = 1.5i_a, \quad v_{2a} = 0.25i_a$$




$$\text{Node 1: } \frac{v_1}{2} = \frac{v_2 - v_1}{5} \rightarrow 0.7v_1 - 0.2v_2 = 0$$

$$\text{Node 2: } i_b = \frac{v_2}{1} + \frac{v_2 - v_1}{5} = -0.2v_1 + 1.2v_2$$

$$\Rightarrow v_{1b} = 0.25i_b, \quad v_{2b} = 0.875i_b$$

$$\text{Superposition: } v_1 = v_{1a} + v_{1b}, \quad v_2 = v_{2a} + v_{2b}$$

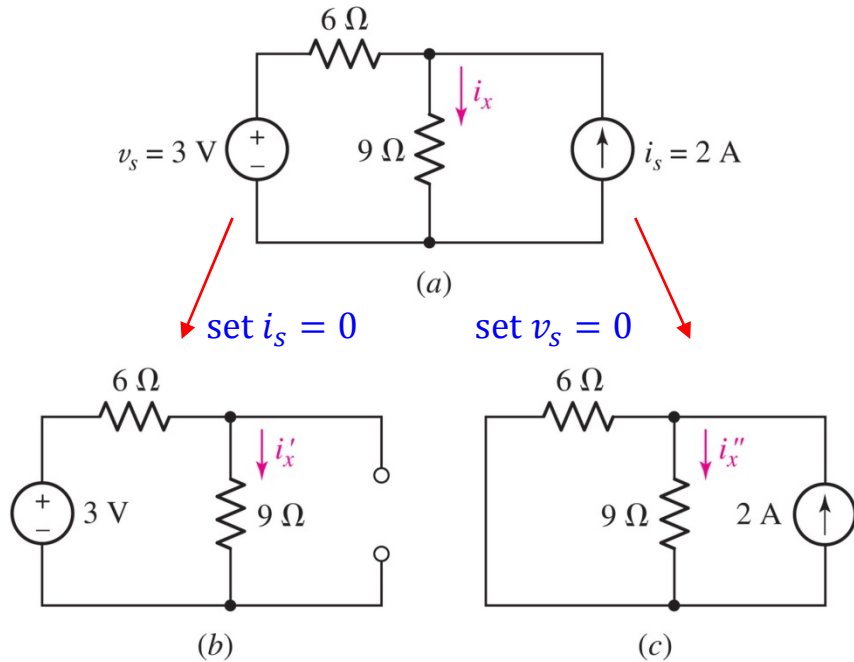Example 5.1 Use superposition to determine the branch current  $i_x$




$$(b) i'_x = \frac{3}{6+9} = \frac{3}{15} A$$

$$(c) i''_x = \frac{6}{6+9} i_s = \frac{6}{15} 2 = \frac{12}{15} A$$

(by current division)

$$\Rightarrow i_x = i'_x + i''_x = \frac{3}{15} + \frac{12}{15} = 1 A$$

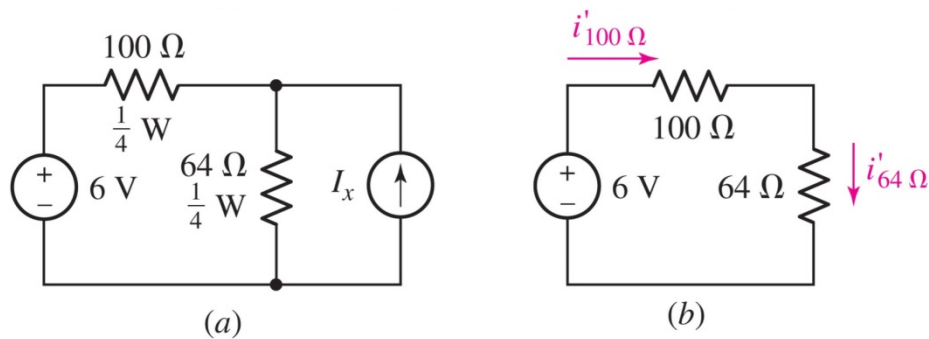
Example 5.2 Determine the maximum *positive* current to which the source  $I_x$  can be set.



$$(b) i'_{100\Omega} = i'_{64\Omega} = \frac{6}{100 + 64} = \frac{6}{164} \text{ mA}$$

$$(c) i''_{100\Omega} = \frac{64}{100 + 64} I_x,$$
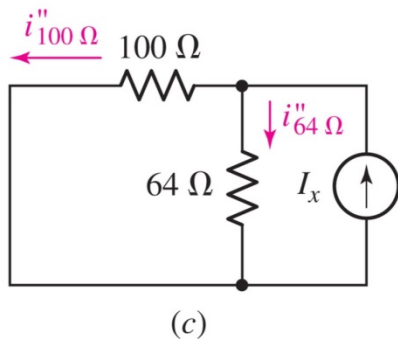
$$i''_{64\Omega} = \frac{100}{100 + 64} I_x$$



$$(a) i_{100\Omega} = -\frac{6}{164} + \frac{64}{164} I_x, \quad \text{positive } I_x$$

$$i_{64\Omega} = \frac{6}{164} + \frac{100}{164} I_x$$

$$i_{100\Omega} = -\frac{6}{164} + \frac{64}{164} I_x < 50 \times 10^{-3}$$

$$\Rightarrow I_x < (86.59 \times 10^{-3}) \left( \frac{164}{64} \right) = 222 \text{ mA}$$

$$i_{64\Omega} = \frac{6}{164} + \frac{100}{164} I_x < 62.5 \times 10^{-3}$$

$$\Rightarrow I_x < (25.91 \times 10^{-3}) \left( \frac{164}{100} \right) = 42.5 \text{ mA}$$




$$I_{x\_max} = 42.5 \text{ mA}$$

$$P = i^2 R \rightarrow i^2 = \frac{P}{R}$$

$$\Rightarrow i_{\max(100\Omega)} = \sqrt{\frac{P_{\max}}{R}} = \sqrt{\frac{1/4}{100}} = 50 \text{ mA}$$

$$\Rightarrow i_{\max(64\Omega)} = \sqrt{\frac{P_{\max}}{R}} = \sqrt{\frac{1/4}{64}} = 62.5 \text{ mA}$$

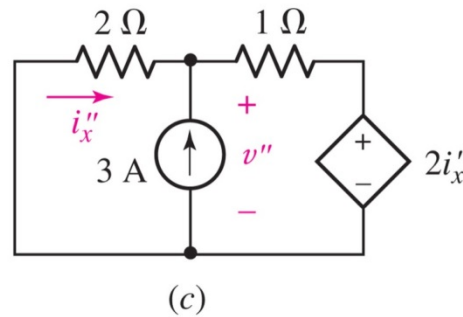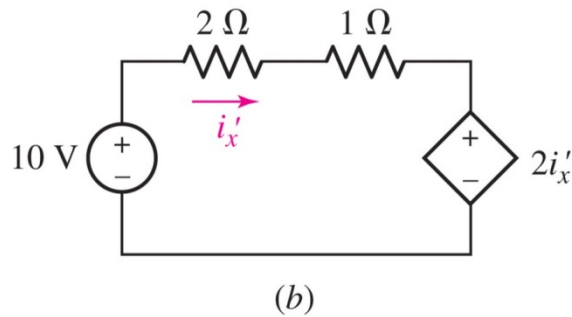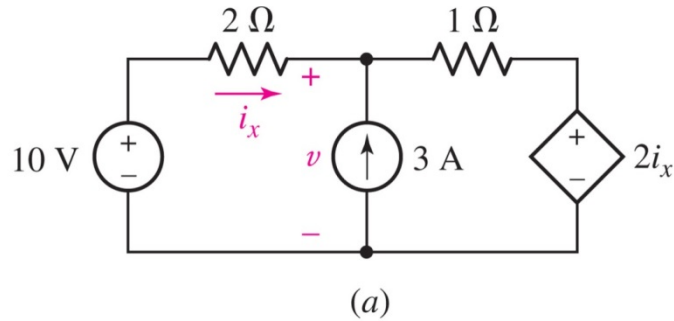**Example 5.3** Use the superposition principle to determine the current  $i_x$



$$(b) \quad -10 + 2i'_x + i'_x + 2i'_x = 0$$

$$\rightarrow i'_x = 2 \text{ A}$$

$$(c) \quad \frac{0 - v''}{2} + 3 + \frac{2i''_x - v''}{1} = 0$$

$$\rightarrow i''_x + 3 + 2i''_x + 2i''_x = 0$$


$$\rightarrow i''_x = -0.6 \text{ A}$$

$$v'' = -2i''_x$$




$$\therefore i_x = i'_x + i''_x = 2 - 0.6 = 1.4 \text{ A}$$

- Practical Voltage Sources




ideal 12 V voltage source

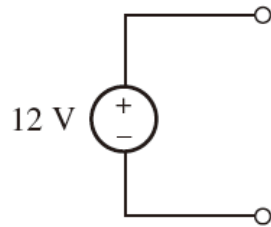

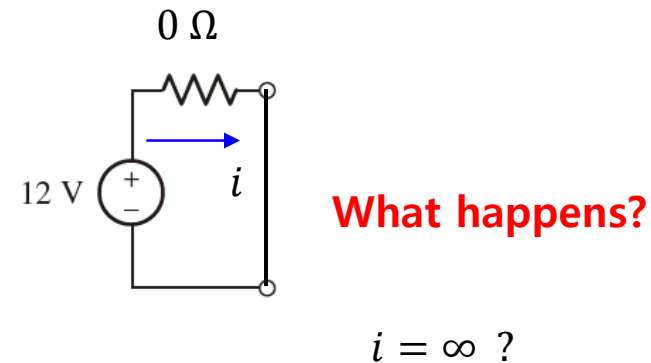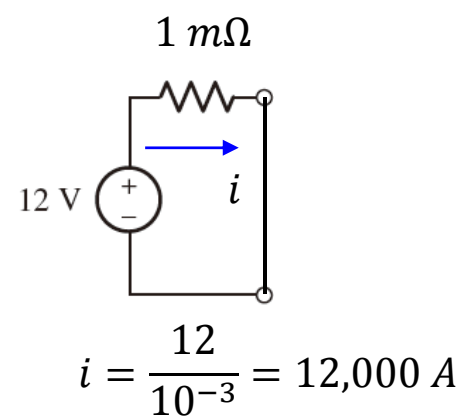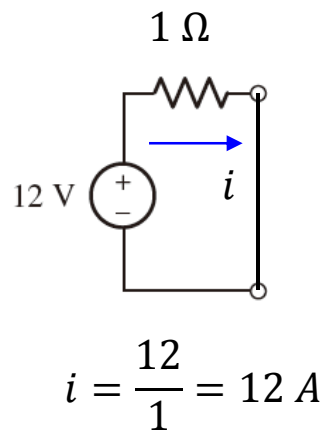independent of the current flowing through them




practical 12 V voltage source

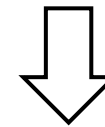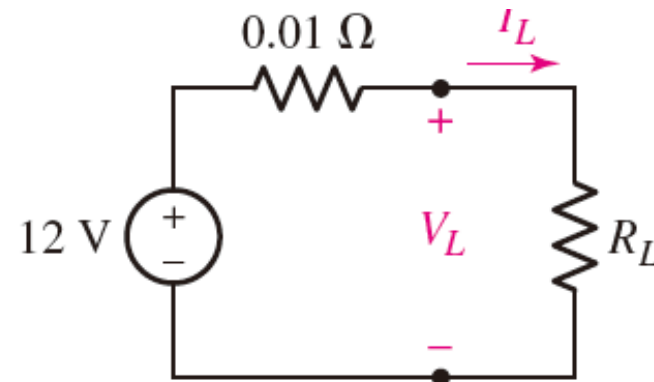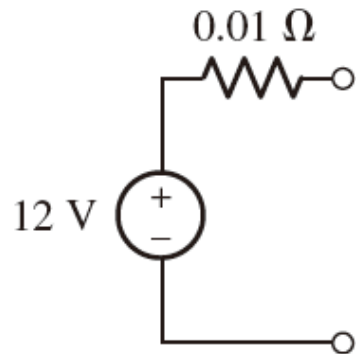


$$-12 + 0.01I_L + V_L = 0$$

$$\rightarrow V_L = -0.01I_L + 12$$
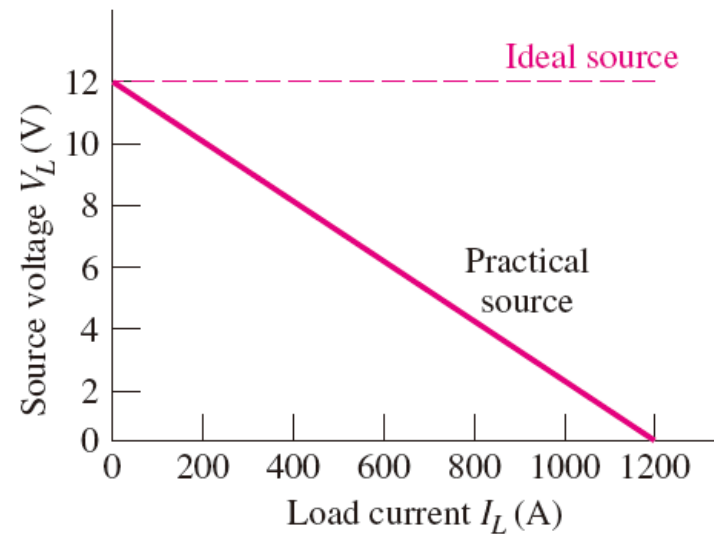
$$\rightarrow V_L = -0.01 \frac{12}{R_L + 0.01} + 12$$





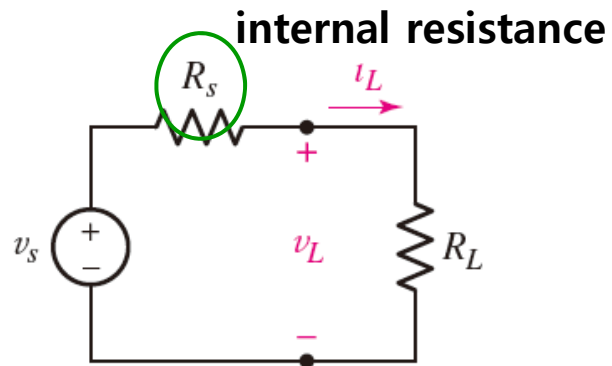


$$-v_s + i_L R_s + v_L (= i_L R_L) = 0$$

$$\rightarrow v_L = v_s - i_L R_s$$


$$\rightarrow i_L = \frac{v_s - v_L}{R_s}$$

$R_L = \infty$  (open circuit)  
 $\Rightarrow i_L = 0$   
 $v_{Loc} = v_s$  **open circuit voltage**

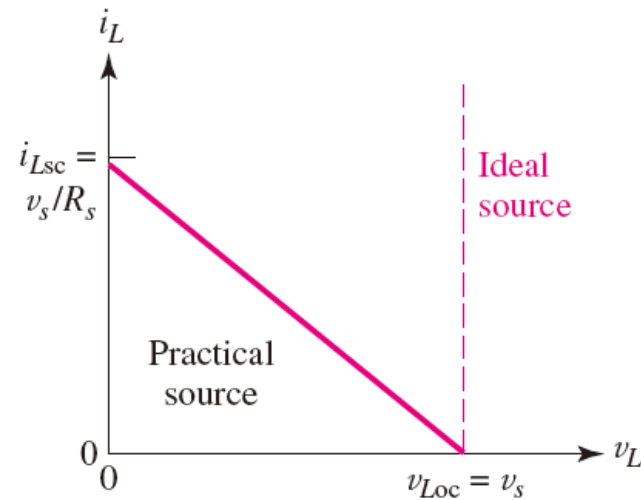$R_L = 0$  (short circuit)  
 $\Rightarrow v_L = 0$   
 $i_{Lsc} = \frac{v_s}{R_s}$  **short circuit current**



- Practical Current Sources

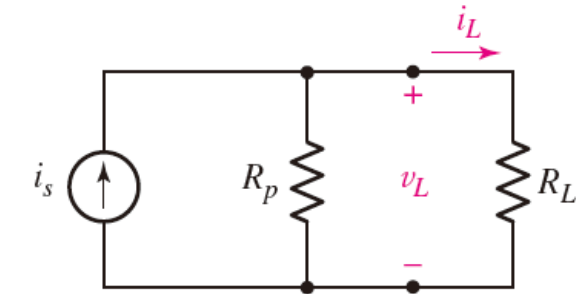

$$i_L = i_s - \frac{v_L}{R_p}$$

$$R_L = \infty \text{ (open circuit)}$$


$$i_L = 0$$

$$v_{Loc} = i_s R_p \quad \text{open circuit voltage}$$


$$R_L = 0 \text{ (short circuit)}$$

$$v_L = 0$$
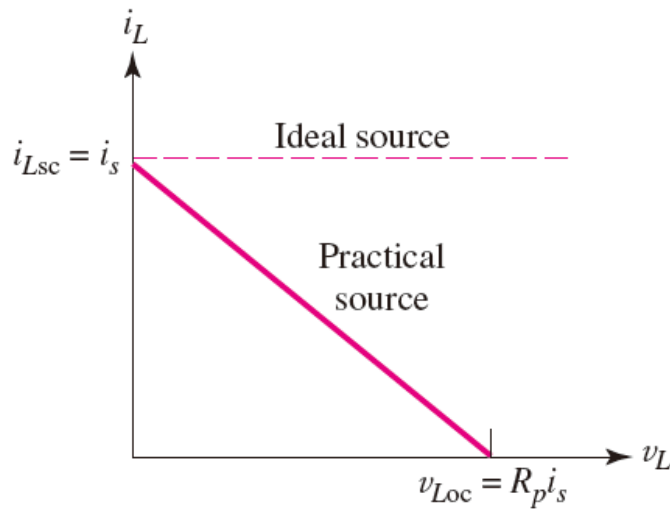
$$i_{Lsc} = i_s \quad \text{short circuit current}$$





- Equivalent Practical Sources

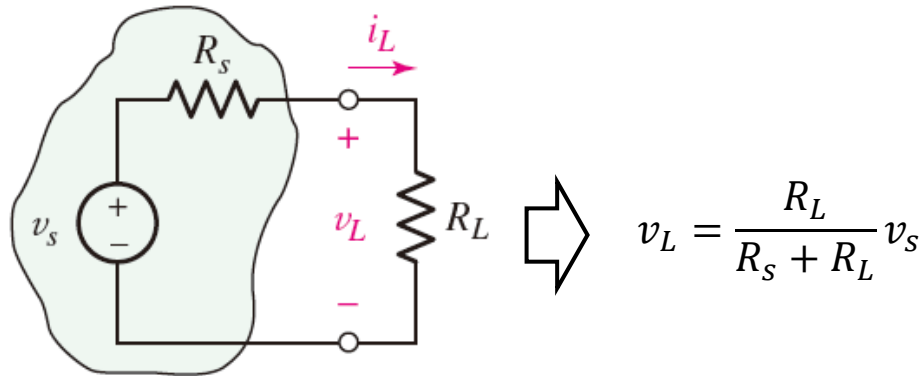


equivalent if

$$R_s = R_p$$

$$v_s = i_s R_p = i_s R_s$$

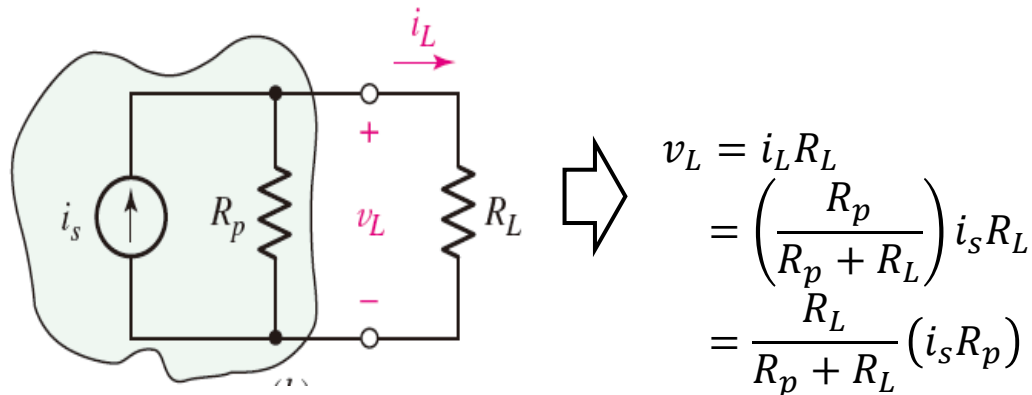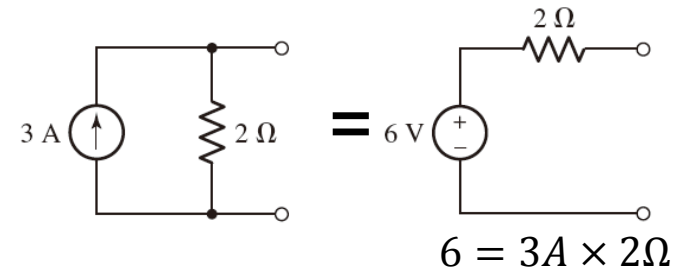

- Equivalent Practical Sources

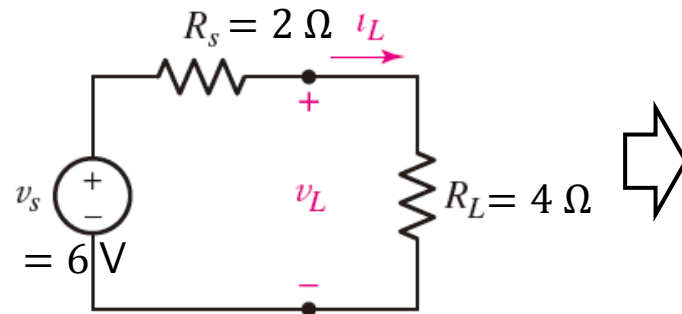

$$v_L = \frac{4}{2+4} 6 = 4 V$$


$$i_L = \frac{6}{2+4} = 1 A$$

$$p_{R_L} = 4 W$$

$$p_{v_s} = v_s i_L = 6 \times 1 = 6 W$$

$$p_{R_s} = 2 \times 1^2 = 2 W$$

Equivalent  
at load

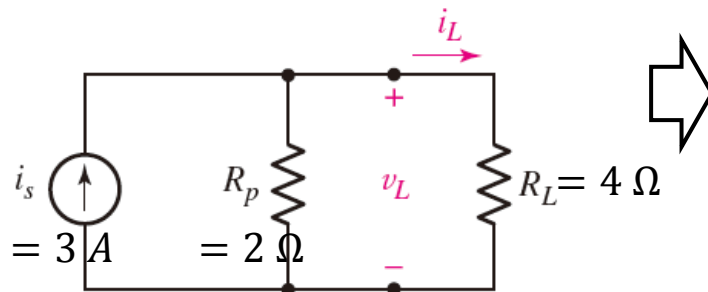

$$v_L = \frac{2}{2+4} (3 \times 4) = 4 V$$



$$i_L = \frac{2}{2+4} 3 = 1 A$$

$$p_{R_L} = 4 W$$

$$p_{i_s} = v_L i_s = 4 \times 3 = 12 W$$

$$p_{R_p} = (3 - 1) \times 2^2 = 8 W$$

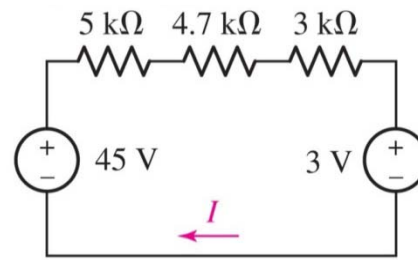
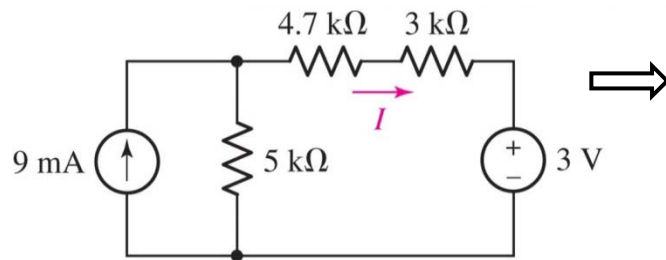
**Example 5.4** Compute the current through the 4.7 kΩ resistor



$$-45 + (5k + 4.7k + 3k)I + 3 = 0$$

$$\rightarrow I = \frac{42}{5k + 4.7k + 3k} = 3.307 \text{ mA}$$

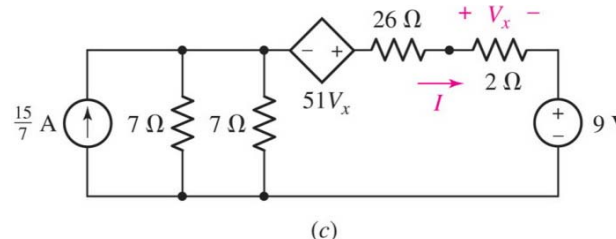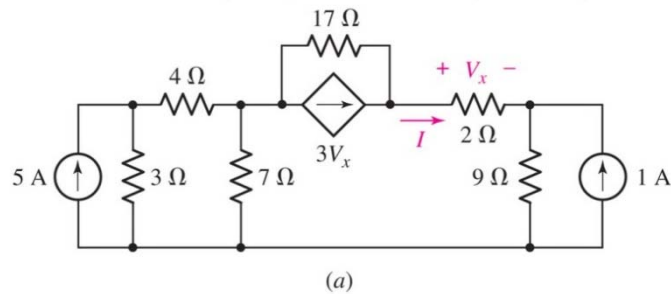**Example 5.5** Calculate the current through the 2 Ω resistor





$$-7.5 + 3.5I - 51V_x + 26I + 2I + 9 = 0$$


$$(V_x = 2I)$$

$$\Rightarrow 31.5I - 51(2I) = -1.5$$

$$\rightarrow I = \frac{1.5}{102 - 31.5}$$

$$= 21.28 \text{ mA}$$

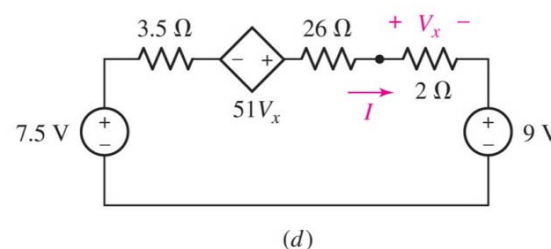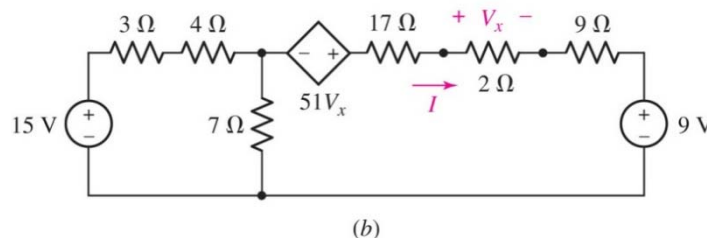

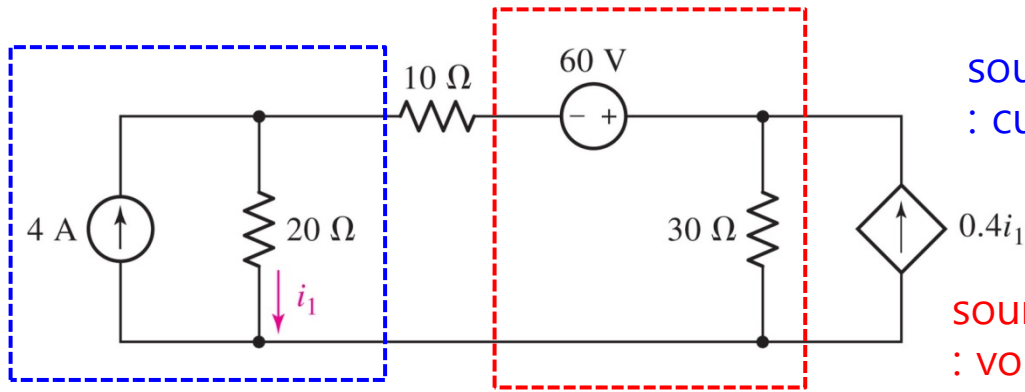


source transformation: OK!


: current source and resistor are in parallel

source transformation: invalid!

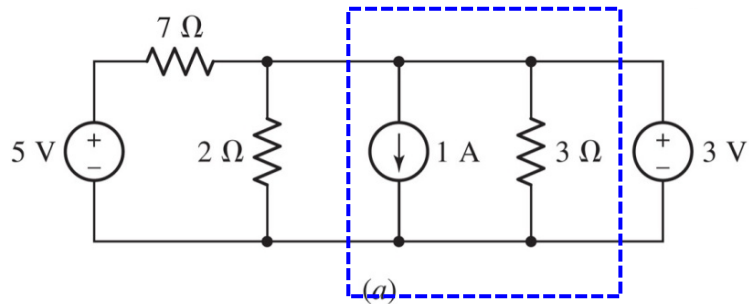
: voltage source and resistor are NOT in series



(a)

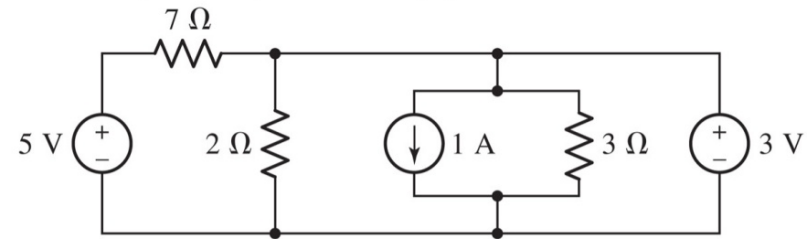


(b)

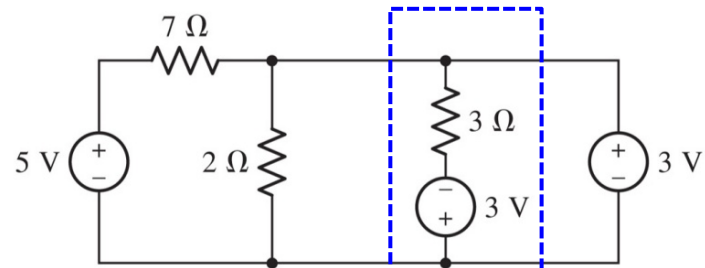

(c)


- Unusual Cases

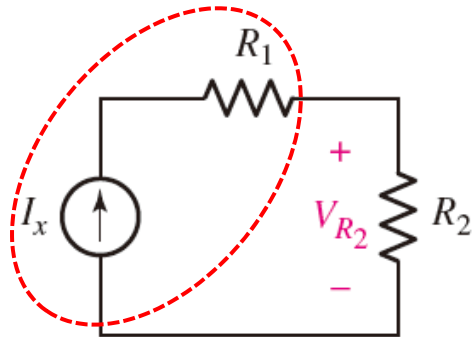

Current source and resistor are in series

Regardless of  $R_1$  value, may omit  $R_1$




$$V_{R_2} = I_x R_2$$

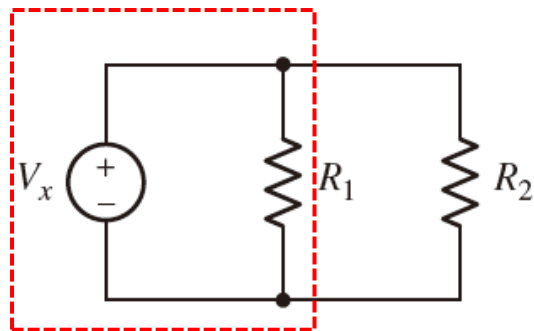




Voltage source and resistor are in parallel

$R_1$  does not alter the voltage across, the current through, or the power dissipated by  $R_2$
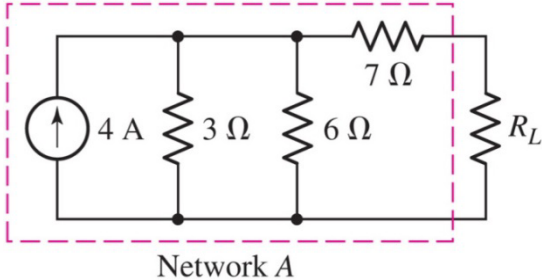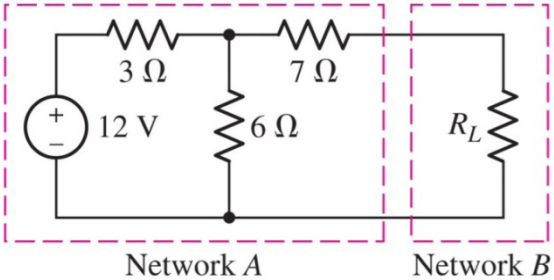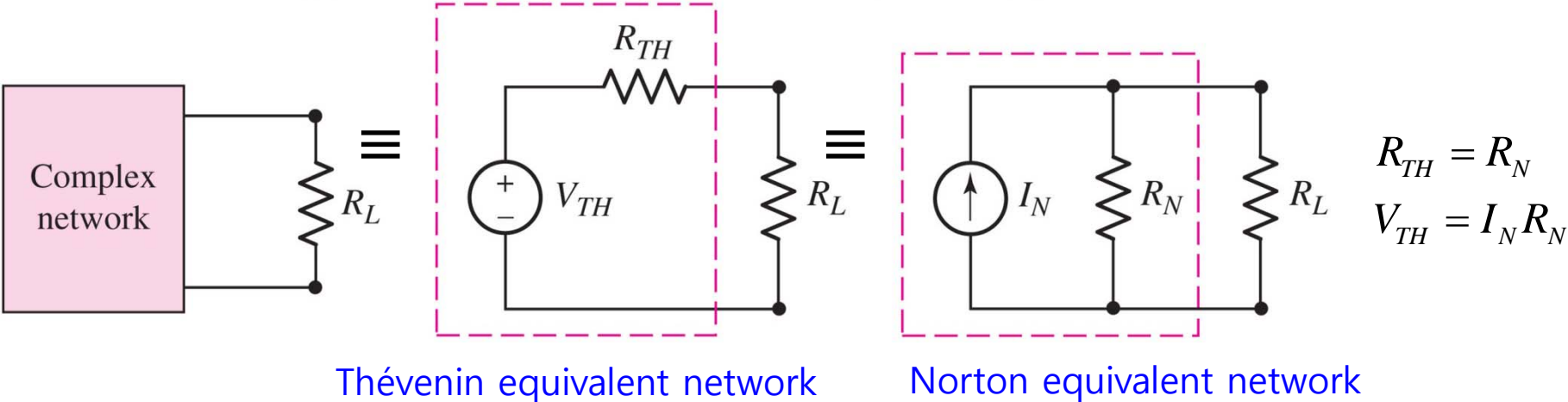
### 5.3 Thévenin and Norton Equivalent Circuits



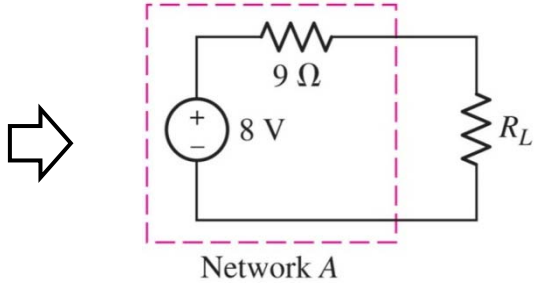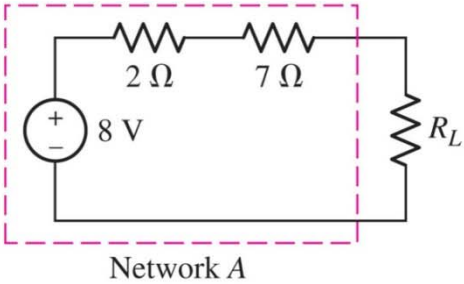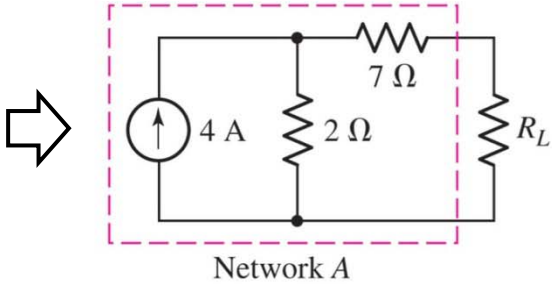**Voltage, current, and power at the load is maintained !!!**





- Thévenin's Theorem

1. Given any linear circuit, rearrange it in the form of two networks, A and B, connected by two wires. A is the network to be simplified; B will be left untouched.
2. Disconnect network B. Define a voltage  $V_{oc}$  as the voltage now appearing across the terminals of network A.
3. Turn off or "zero out" every independent source in the network A to form an inactive network. Leave dependent sources unchanged.
4. Connect an independent voltage source with value  $V_{oc}$  in **series** with the inactive network. Do now complete the circuit; leave the two terminals **disconnected (open)**.
5. Connect network B to the terminals of the new network A. All currents and voltages in B will remain unchanged.
6. The only restriction that we must impose on A or B is that all dependent sources in A have their control variables in A, and similarly for B
7. The inactive network A can be represented by a single equivalent resistance  $R_{TH}$ , which we will call the *Thévenin equivalent resistance*.


- Norton's Theorem

1. Given any linear circuit, rearrange it in the form of two networks, A and B, connected by two wires. Network A is the network to be simplified; B will be left untouched. As before, if either network contains a dependent source, *its controlling variable must be in the same network*
2. Disconnect network B and short the terminals of A. Define a current  $i_{sc}$  as the current now flowing through the shorted terminals of network A.
3. Turn off or "zero out" every independent source in the network A to form an inactive network. Leave dependent sources unchanged.
4. Connect an independent voltage source with value  $i_{sc}$  in **parallel** with the inactive network. Do now complete the circuit; leave the two terminals **disconnected**.
5. Connect network B to the terminals of the new network A. All currents and voltages in B will remain unchanged.


$$v_{oc} = R_{TH}i_{sc}$$

### 5.3 Thévenin and Norton Equivalent Circuits

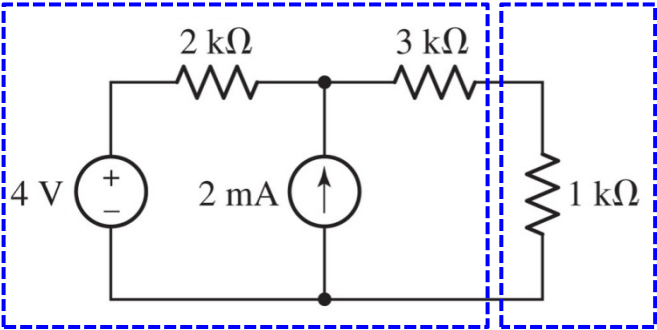**Example 5.8** Find the Thévenin and Norton equivalent circuits, faced by the 1 kΩ resistor.




Network A                      Network B

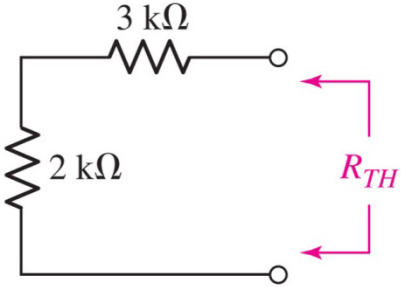

Zero-out the independent sources in network A.

$$R_{TH} = 3 + 2 = 5 \Omega$$

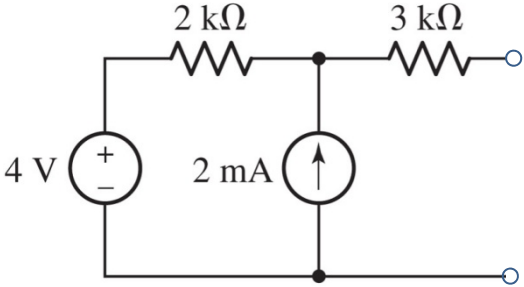


$$V_{OC} = V_{OC|4V} + V_{OC|2mA}$$


$$V_{OC|4V} = 4 V$$

$$V_{OC|2mA} = (2 \times 10^{-3})(2 \times 10^3) = 4 V$$

$$\rightarrow V_{OC} = V_{OC|4V} + V_{OC|2mA} = 4 + 4 = 8 V$$

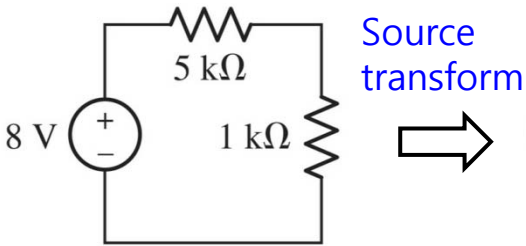


Source transform

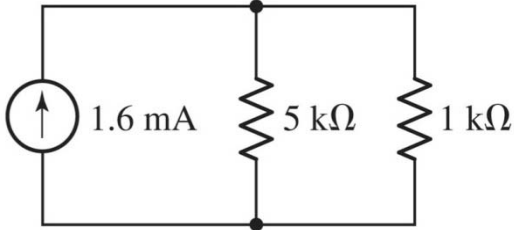

Thévenin equivalent network

Norton equivalent network

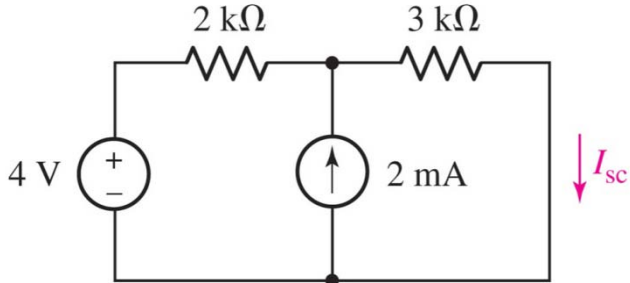


$$I_{SC} = I_{SC|4V} + I_{SC|2mA}$$

$$= \frac{4}{2+3} + \frac{2}{2+3} \cdot 2 = \frac{8}{5} A$$

- When Dependent sources are present

- Controlling variable and its associated element(s) should be in the same network.

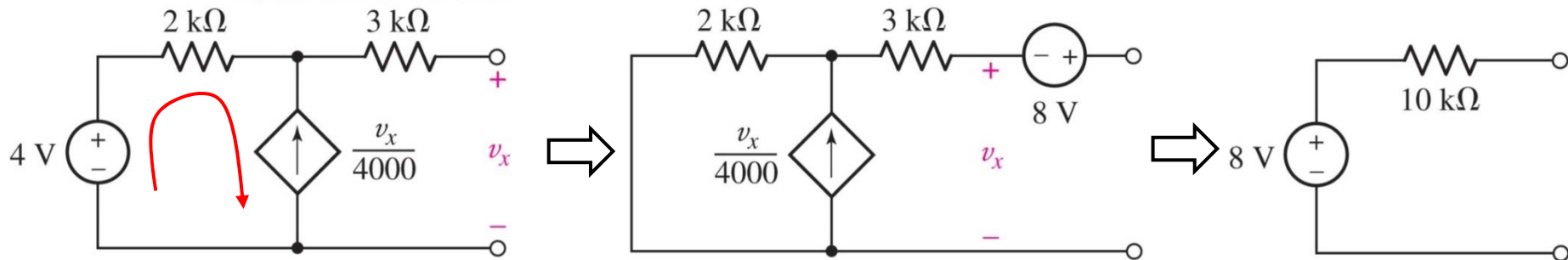Example 5.9 Determine the Thévenin equivalent circuits




$$-4 + 2 \times 10^3 \left( -\frac{v_x}{4000} \right) + v_x = 0$$

$$\rightarrow v_x = v_{OC} = V_{TH} = 8V$$

Useless form of Thévenin circuit

$$v_{OC} = R_{TH} i_{SC}$$


- Finding  $R_{TH}$

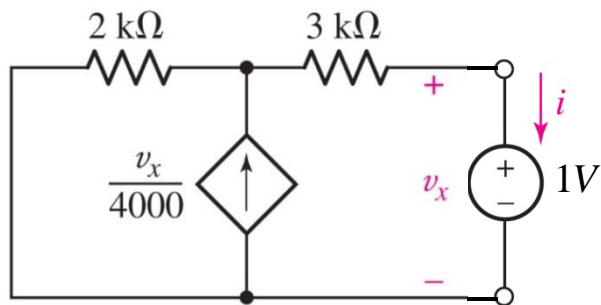


$$v_x = 1V$$

$$i = \frac{1}{4000} \times \frac{2}{3+2} = 0.1mA$$


$$R_{TH} = \frac{1V}{i} = 10k\Omega$$

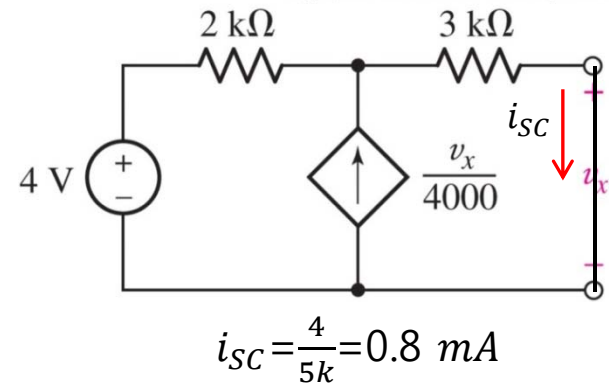

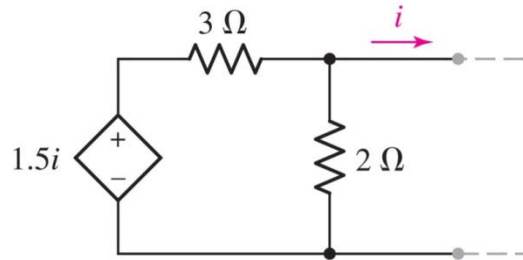
Example 5.10 Determine the Thévenin equivalent circuits (No independent source)


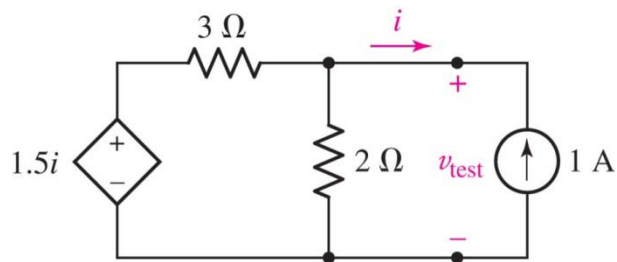
$$\begin{aligned} v_{oc} &= 0 \\ i_{sc} &= 0 \end{aligned} \implies R_{TH} = \frac{0}{0} : \text{Too much answer}$$




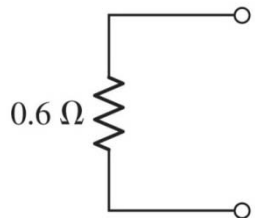
$$\begin{aligned} 1 &= \frac{v_{test}}{2} + \frac{v_{test} - 1.5i}{3} \\ \rightarrow 6 &= 3v_{test} + 2v_{test} - 1.5 \times (-1) \times 2 \\ \rightarrow v_{test} &= \frac{3}{5} V \end{aligned}$$



$$R_{TH} = \frac{v_{test}}{1 A} = 0.6\Omega$$

- Digital Multimeter: Voltage

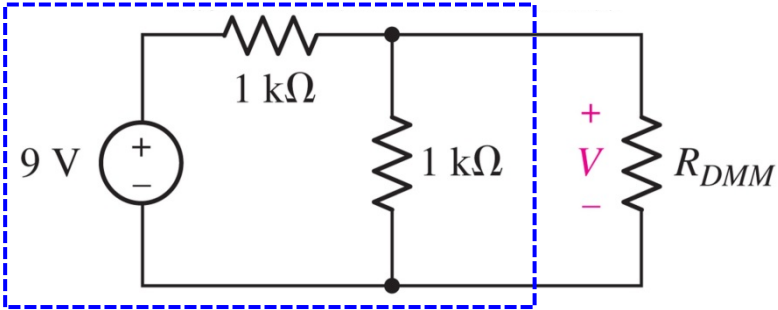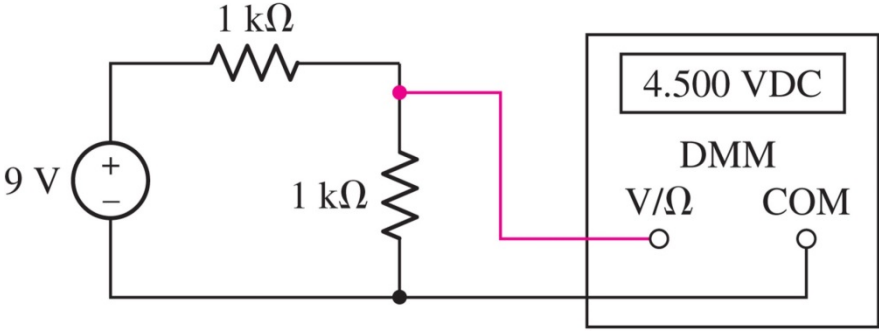

$$R_{TH} = 1 || 1 = 500 \Omega$$

$$V_{OC} = \frac{1}{1+1} 9 = 4.5 V$$

$$V = \frac{R_{DMM}}{R_{TH} + R_{DMM}} V_{OC}$$

$$= \frac{10 \times 10^6}{500 + 10 \times 10^6} 4.5 = 4.4998 V$$


- Digital Multimeter: Current

$$-9 + 1000I + R_{DMM}I + 1000I = 0$$

$$\rightarrow I = \frac{9}{2000 + R_{DMM}}$$

$$R_{DMM} = 0.1 \Omega \rightarrow I = 4.4998 \text{ mA}$$


Less than 4.5 mA (ideal value)

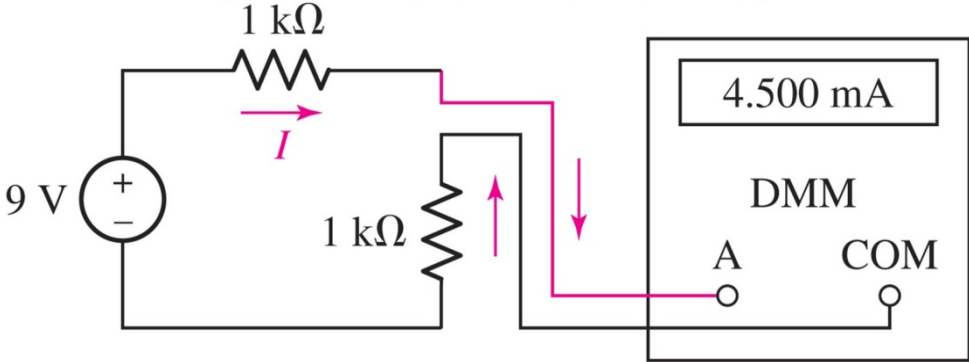

Ideal DMM  
 $R_{DMM} = 0$  for current measurement  
 $R_{DMM} = \infty$  for voltage measurement

- Digital Multimeter: Resistance

DMM actually measure  $R || R_{DMM}$

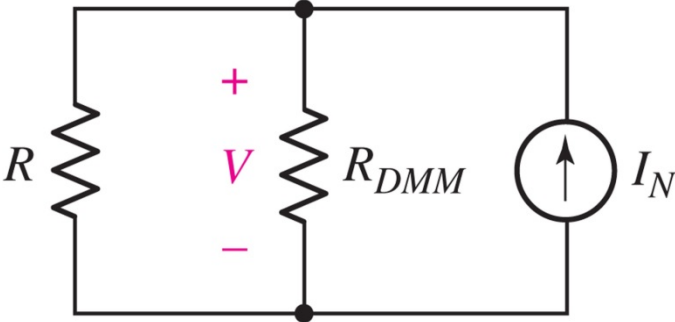

$$V = (R || R_{DMM}) I_N$$

$$R_{DMM} = 10 \text{ M}\Omega$$

$$R = 10 \Omega$$


$$\rightarrow R_{DMM} || R = 9.9999 \Omega$$

$$R_{DMM} = 10 \text{ M}\Omega$$

$$R = 10 \text{ M}\Omega$$

$$\rightarrow R_{DMM} || R = 5 \text{ M}\Omega$$

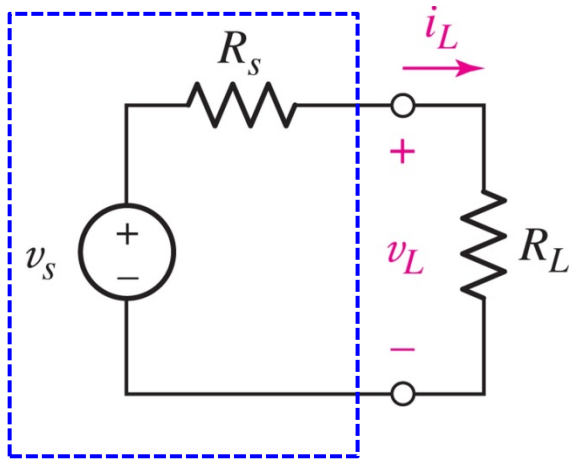- An independent voltage source in series with a resistance  $R_s$ , or an independent current source in parallel with a resistance  $R_s$ , delivers maximum power to a load resistance  $R_L$  such that  $R_L = R_s$ .



$$i_L = \frac{v_s}{R_s + R_L}$$

$$p_L = i_L^2 R_L = \frac{R_L v_s^2}{(R_s + R_L)^2}$$

Minimum power transfer

$$\begin{aligned} R_L = 0 &\rightarrow p_L = 0, \\ R_L = \infty &\rightarrow p_L = 0 \end{aligned}$$

$$\begin{aligned} \frac{dp_L}{dR_L} &= \frac{(R_s + R_L)^2 v_s^2 - 2v_s^2 R_L (R_s + R_L)}{(R_s + R_L)^4} = 0 \\ \Rightarrow 2R_L (R_s + R_L) &= (R_s + R_L)^2 \end{aligned}$$


$$\Rightarrow R_L = R_s \quad \text{Condition for maximum power transfer}$$

$$\begin{aligned} R_{TH} &= R_s \\ V_{TH} &= v_s \end{aligned}$$


$$p_L = \frac{R_s v_s^2}{(R_s + R_s)^2} = \frac{v_s^2}{4R_s} = \frac{v_{TH}^2}{4R_{TH}}$$



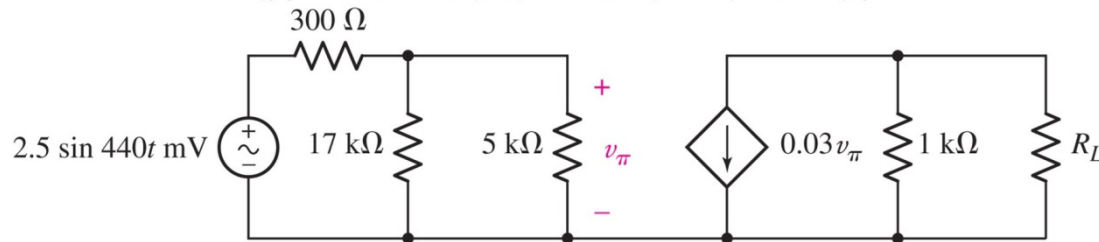**Example 5.11** Choose a load resistance so that maximum power is transferred.




$$R_{TH} = 1 \text{ k}\Omega$$

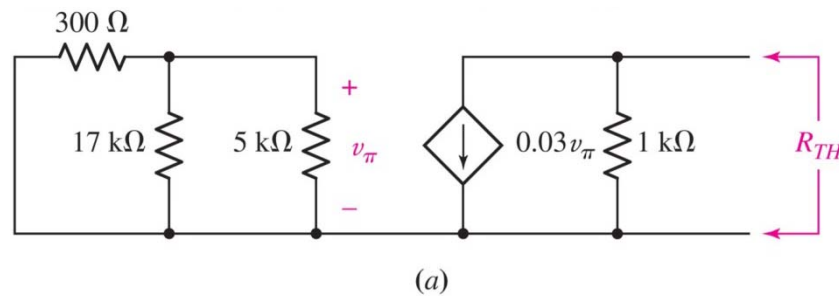

$$v_{oc} = 1 \text{ k} \times (-0.03v_{\pi}) = -30v_{\pi}$$




$$v_{\pi} = \frac{17||5}{0.3+17||5} (2.5 \sin 440t) \text{ mV}$$
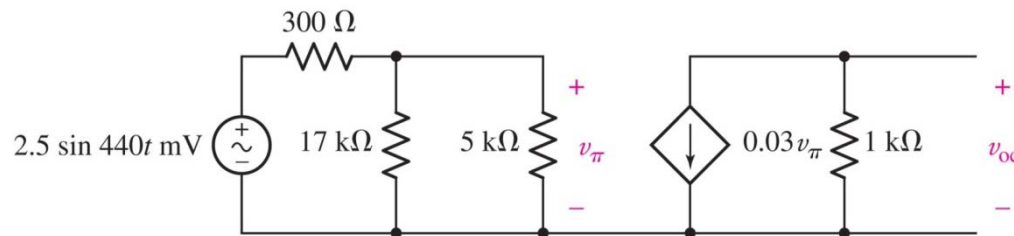
$$\Rightarrow v_{oc} = -69.6 \sin 440t \text{ mV}$$



$$p_{max} = \frac{v_{oc}^2}{4R_{TH}} = 1.211 \sin^2 440t \text{ }\mu\text{W}$$


## 5.5 Delta-Wye Conversion

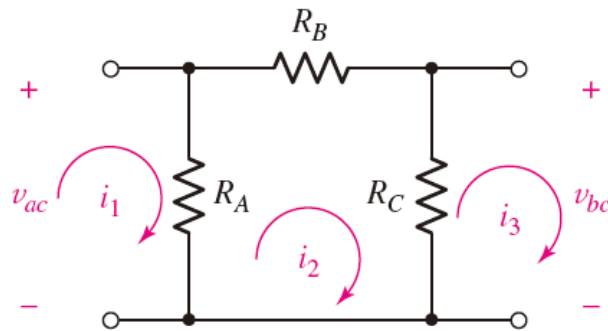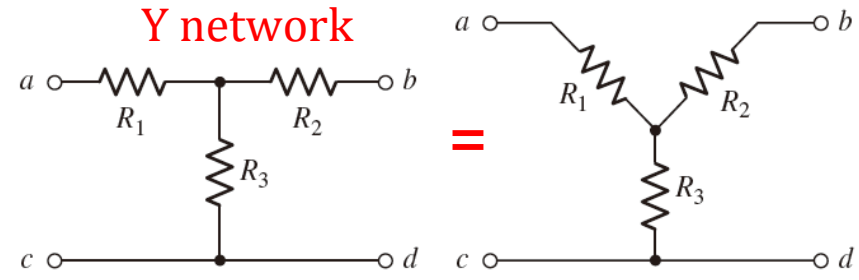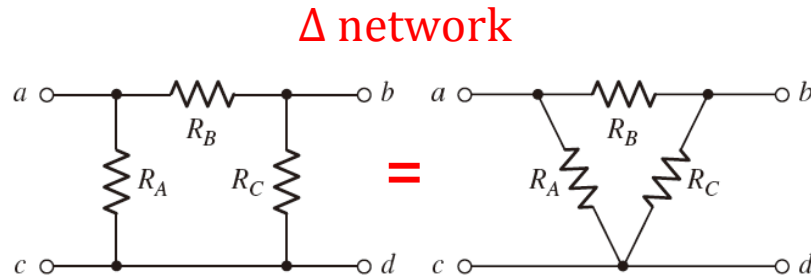

$v_{ac}$ ,  $v_{bc}$ ,  $i_1$ ,  
and  $i_3$  are  
same in both  
networks

$$\begin{aligned} v_{ac} &= R_A(i_1 - i_2) \\ R_A(i_2 - i_1) + R_B i_2 + R_C(i_2 - i_3) &= 0 \\ -v_{bc} &= R_C(i_3 - i_2) \end{aligned}$$

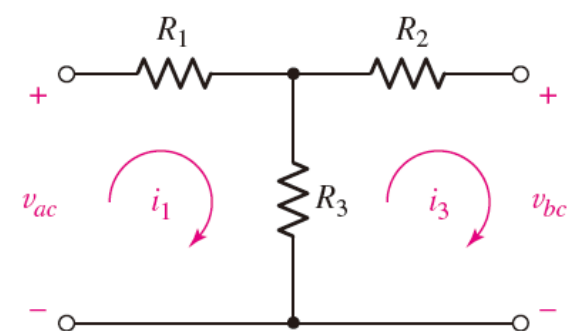
$$\begin{aligned} R_A &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \\ R_B &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \\ R_C &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \end{aligned}$$



$$\begin{aligned} v_{ac} &= R_1 i_1 + R_3(i_1 - i_3) \\ -v_{bc} &= R_2 i_3 - R_3(i_3 - i_1) \end{aligned}$$

$$\begin{aligned} R_1 &= \frac{R_A R_B}{R_A + R_B + R_C} \\ R_2 &= \frac{R_B R_C}{R_A + R_B + R_C} \\ R_3 &= \frac{R_C R_A}{R_A + R_B + R_C} \end{aligned}$$



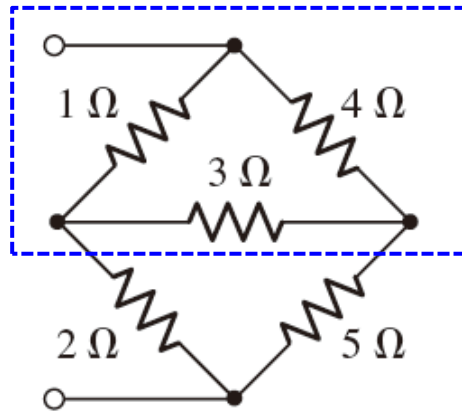
Example 5.12 Find the Thévenin equivalent circuits (using  $\Delta$ -Y conversion)



$$R_1 = \frac{1 \times 3}{1 + 3 + 4} = \frac{3}{8}$$

$$R_2 = \frac{1 \times 3 + 4}{4 \times 1} = \frac{7}{4}$$
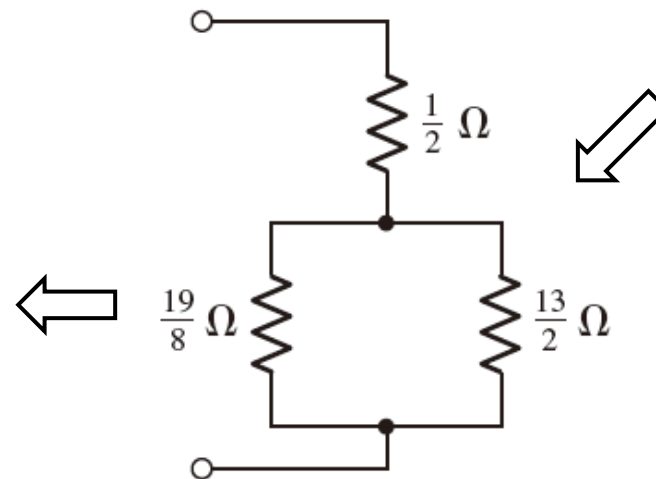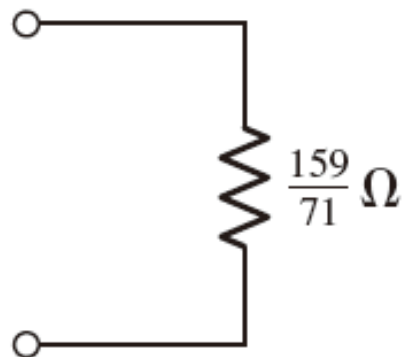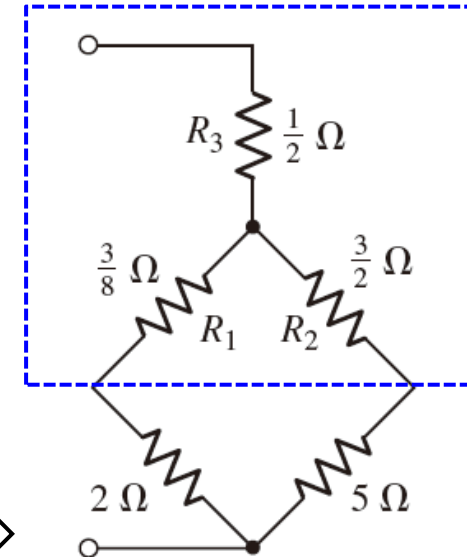
$$R_3 = \frac{1 + 3 + 4}{1 + 3 + 4} = \frac{8}{8} = 1$$



Homework : 5장 Exercises 5의 배수 문제 (70번 문제까지)

- Due day : 5장 수업 끝나고 일주일 후 수업시작 전까지 제출.

---

이 자료에 나오는 모든 그림은 McGraw-hill 출판사로부터 제공받은 그림을 사용하였음.

All figures at this slide file are provided from The McGraw-hill company.