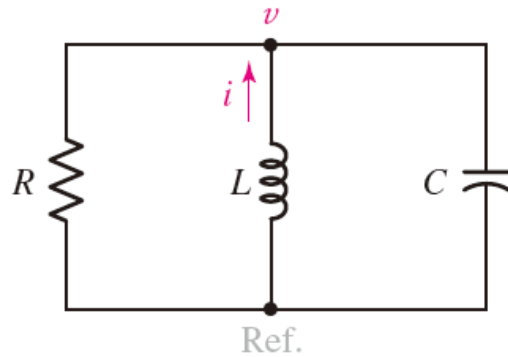

Chapter 9

The *RLC* Circuits

- 9.1 The Source-Free Parallel Circuit
- 9.2 The Overdamped Parallel *RLC* Circuit
- 9.3 Critical Damping
- 9.4 The Underdamped Parallel *RLC* Circuit
- 9.5 The Source-Free Series *RLC* Circuit
- 9.6 The Complete Response of the *RLC* Circuit
- 9.7 The Lossless *LC* Circuit

- Natural response of parallel RLC circuit



$$\frac{v}{R} + \frac{1}{L} \int_{t_0}^t v dt' - i(t_0) + C \frac{dv}{dt} = 0$$

Assume solution :

$$\rightarrow C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0$$

$$v = Ae^{st}$$

Second-order
homogeneous
differential
equation

$$\rightarrow CA s^2 e^{st} + \frac{1}{R} A s e^{st} + \frac{1}{L} A e^{st} = 0$$

$$\rightarrow Ae^{st} \left(Cs^2 + \frac{1}{R}s + \frac{1}{L} \right) = 0$$

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$v_1 = A_1 e^{s_1 t} \Rightarrow C \frac{d^2 v_1}{dt^2} + \frac{1}{R} \frac{dv_1}{dt} + \frac{1}{L} v_1 = 0$$

$$v_2 = A_2 e^{s_2 t} \Rightarrow C \frac{d^2 v_2}{dt^2} + \frac{1}{R} \frac{dv_2}{dt} + \frac{1}{L} v_2 = 0$$

Real or Complex numbers

$$\Rightarrow C \frac{d^2 (v_1 + v_2)}{dt^2} + \frac{1}{R} \frac{d(v_1 + v_2)}{dt} + \frac{1}{L} (v_1 + v_2) = 0$$

$$v(t) = v_1 + v_2 = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

General form of the natural response

- Definition of Frequency Terms

$$s = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

s : real numbers of complex conjugates

unit: sec^{-1} : frequency

$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\rightarrow s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\begin{aligned} \rightarrow v &= Ae^{st} = Ae^{-\alpha \pm \sqrt{\alpha^2 - \omega_0^2}t} \\ &= Ae^{-\alpha t} e^{\pm \sqrt{\alpha^2 - \omega_0^2}t} \end{aligned}$$

exponential
damping
coefficient

resonant
frequency

complex frequency

$$\alpha > \omega_0 \rightarrow \sqrt{\alpha^2 - \omega_0^2} > 0 \Rightarrow s: \text{real roots}$$

overdamped response


$$\alpha = \omega_0 \rightarrow \sqrt{\alpha^2 - \omega_0^2} = 0 \Rightarrow s: \text{multiple real roots}$$

critically damped response

$$\alpha < \omega_0 \rightarrow \sqrt{\alpha^2 - \omega_0^2} < 0 \Rightarrow s: \text{complex roots}$$

underdamped response

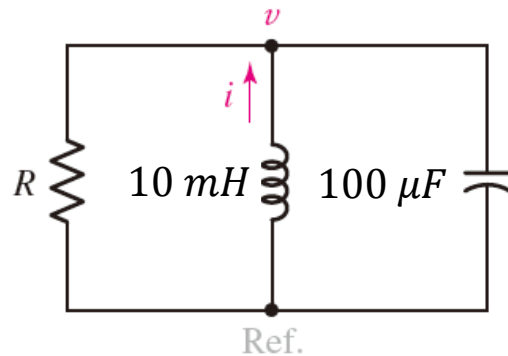Example 9.1 Determine the resistor value for overdamped and underdamped responses.



$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{\frac{1}{(10 \times 10^{-3})(100 \times 10^{-6})}} = 10^3 \text{ rad/s}$$

overdamped case : $\alpha > \omega_0 \rightarrow \frac{1}{2RC} > 10^3 \Rightarrow R < \frac{1}{2 \times 10^3 \times 100 \times 10^{-6}} = 5 \Omega$

underdamped case : $R > 5 \Omega$

- Overdamped parallel RLC circuit

$$\alpha > \omega_0 \Rightarrow \frac{1}{2RC} > \frac{1}{\sqrt{LC}} \Rightarrow LC > 4R^2C^2$$


s_1, s_2 : negative real number

$$\sqrt{\alpha^2 - \omega_0^2} < \alpha$$

$$\Rightarrow \underbrace{(-\alpha - \sqrt{\alpha^2 - \omega_0^2})}_{s_1} < \underbrace{(-\alpha + \sqrt{\alpha^2 - \omega_0^2})}_{s_2} < 0$$

$$v(t) \Big|_{t \rightarrow \infty} = A_1 e^{s_1 t} + A_2 e^{s_2 t} \Big|_{t \rightarrow \infty} \rightarrow 0$$

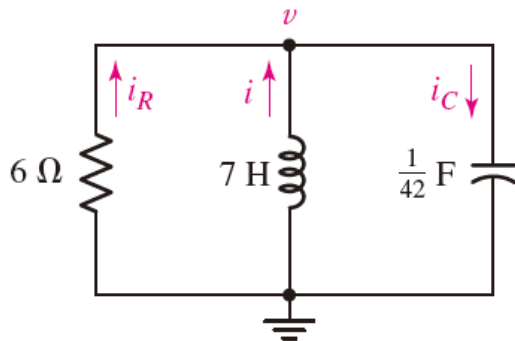The constants A_1 and A_2 are determined by the initial conditions.



$$v(0) = 0 \text{ V}, i(0) = 10 \text{ A}$$

$$v(t) = A_1 e^{-t} + A_2 e^{-6t}$$

$$v(0) = A_1 + A_2 = 0$$

$$i_C = C \frac{dv}{dt}$$

$$\begin{aligned} \rightarrow \frac{dv}{dt} \Big|_{t=0} &= \frac{i_C(0)}{C} = \frac{i_R(0) + i(0)}{C} \\ &= \frac{10}{\frac{1}{42}} = 420 \text{ V/s} \end{aligned}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 6 \times \frac{1}{42}} = 3.5 \text{ s}^{-1},$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{7 \times \frac{1}{42}}} = \sqrt{6} \text{ s}^{-1},$$

$$s_1 = -1, s_2 = -6$$

$$\frac{dv}{dt} = -A_1 e^{-t} - 6A_2 e^{-6t} \Rightarrow \frac{dv}{dt} \Big|_{t=0} = -A_1 - 6A_2$$


$$A_1 + A_2 = 0$$

$$-A_1 - 6A_2 = 420$$


$$\Rightarrow A_1 = 84, A_2 = -84$$

$$\therefore v(t) = 84(e^{-t} - e^{-6t})$$

- Natural response of Overdamped parallel RLC circuit

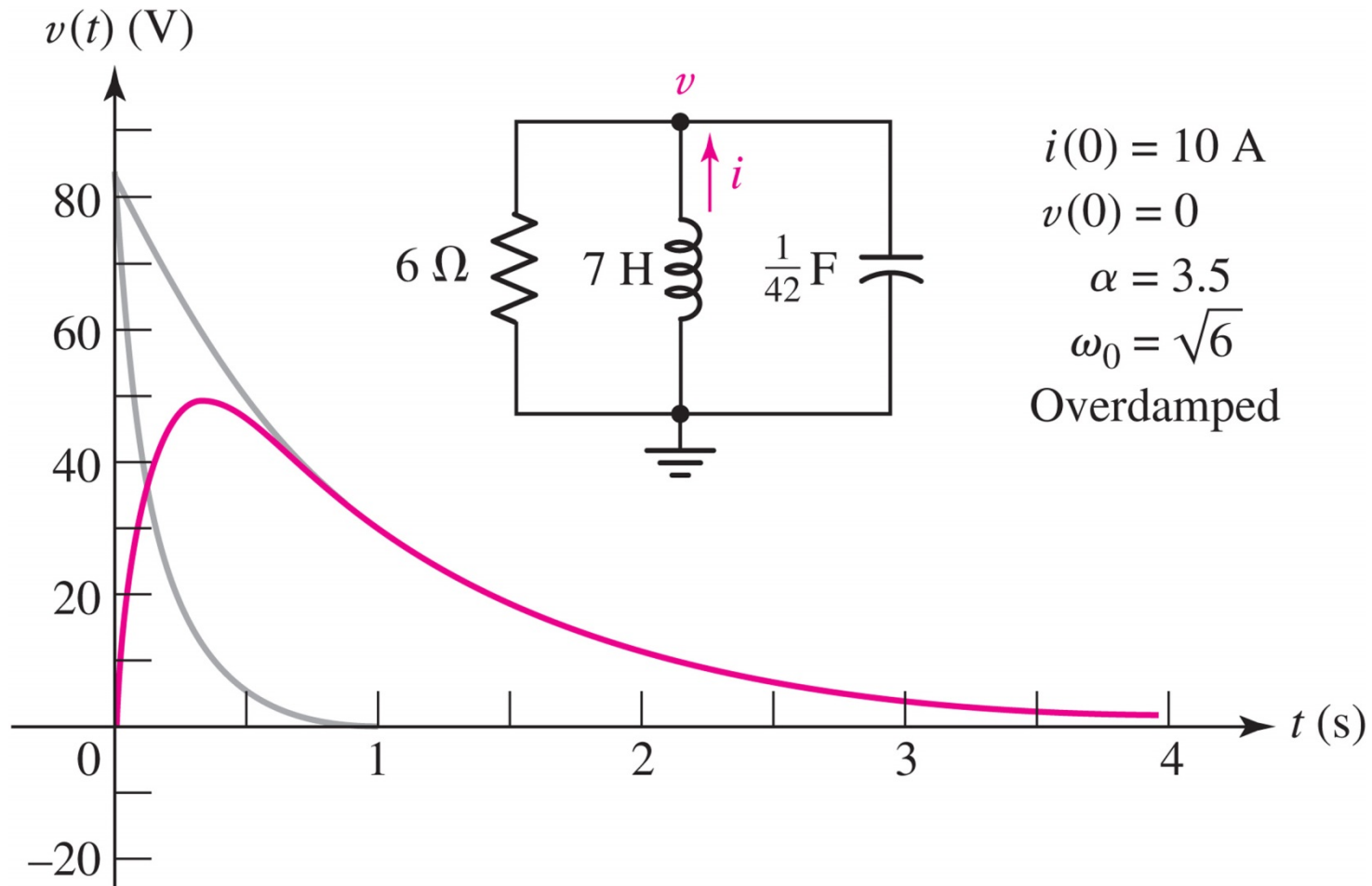

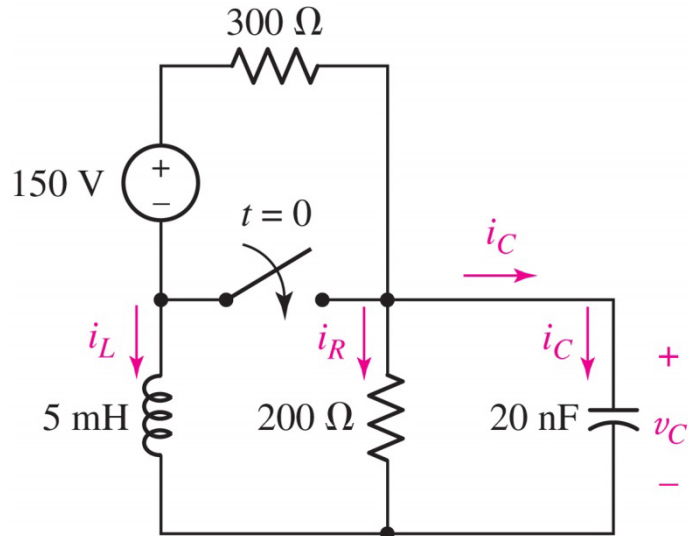Example 9.2 Find an expression for $v_C(t)$ for $t > 0$.



$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 200 \times 20 \times 10^{-9}} = 125,000 \text{ s}^{-1}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times 10^{-3} \times 20 \times 10^{-9}}} = 100,000 \text{ rad/s}$$

$\alpha > \omega_0$: overdamped response

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -50,000 \text{ s}^{-1},$$


$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -200,000 \text{ s}^{-1},$$

$t > 0$

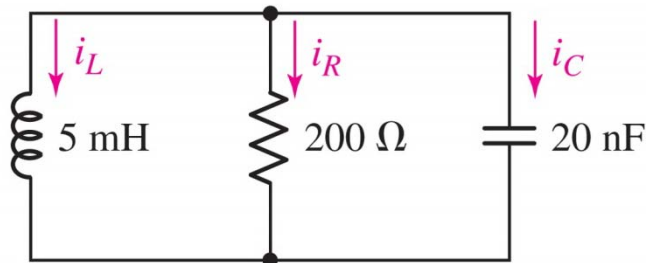

$$\Rightarrow v_C(t) = A_1 e^{-50000t} + A_2 e^{-200000t}$$

Example 9.2 continued...

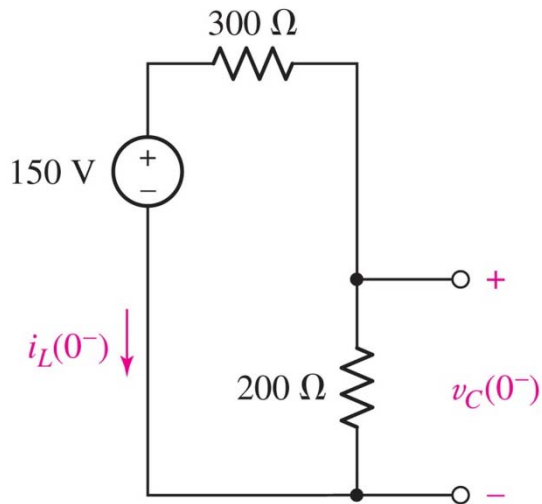

$$v_C(t) = A_1 e^{-50000t} + A_2 e^{-200000t} \quad t > 0$$

$$i_L(0^-) = -\frac{150}{300 + 200} = -0.3 \text{ A}$$

$$\Rightarrow v_C(0^-) = \frac{200}{300 + 200} 150 = 60 \text{ V}$$


$$\Rightarrow v_C(0^+) = A_1 + A_2 = 60$$

$$i_C = C \frac{dv_C}{dt}$$

$$\rightarrow \left. \frac{dv_C}{dt} \right|_{t=0^+} = \frac{i_C(0^+)}{C} = \frac{-i_R(0^+) - i_L(0^+)}{C}$$

$$= \frac{-\frac{v_C(0^+)}{200} - (-0.3)}{20 \times 10^{-9}} = \frac{-\frac{60}{200} + 0.3}{20 \times 10^{-9}} = 0$$



$$\therefore -50000A_1 - 200000A_2 = 0$$

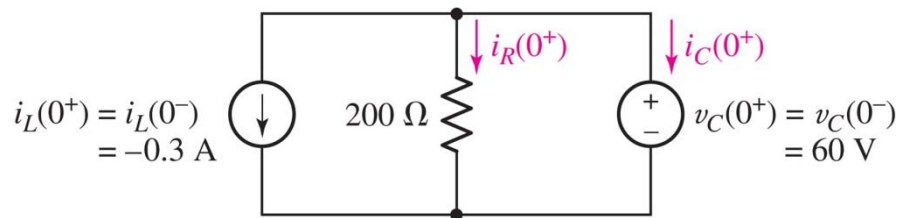

$$\Rightarrow A_1 = 80, A_2 = -20$$

$$\therefore v_C(t) = 80e^{-50000t} - 20e^{-200000t} \text{ V}, \quad t > 0$$

Example 9.3 Express i_R for all time

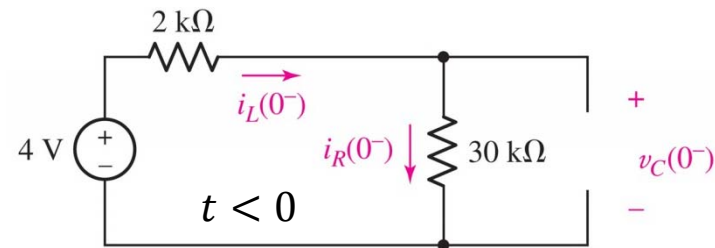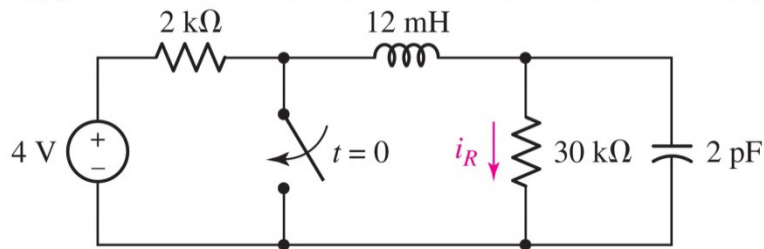

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 30 \times 10^3 \times 2 \times 10^{-12}} = 8.33 \times 10^6 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{12 \times 10^{-3} \times 2 \times 10^{-12}}} = 6.45 \times 10^6 \text{ rad/s}$$

$\alpha > \omega_0$: overdamped response

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -3.063 \times 10^6 \text{ s}^{-1},$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -13.60 \times 10^6 \text{ s}^{-1},$$

Let $i_R(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$


$$i_R(0^-) = i_L(0^-) = \frac{4}{32 \times 10^3} = 125 \times 10^{-6} \text{ A} \quad \rightarrow \quad v_C(0^-) = (30 \times 10^3)(125 \times 10^{-6}) = 3.75 \text{ V}$$

$$i_R(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \Rightarrow i_R(0^+) = A_1 + A_2 = 125 \times 10^{-6} \quad \therefore v_C(0^-) = v_C(0^+)$$

$$v_C(t) = 30k \times i_R(t)$$


$$i_C = C \frac{dv_C}{dt} \rightarrow \left. \frac{dv_C}{dt} \right|_{t=0^+} = \frac{i_C(0^+)}{C} = \frac{-i_R(0^+) + i_L(0^+)}{C} = 0$$
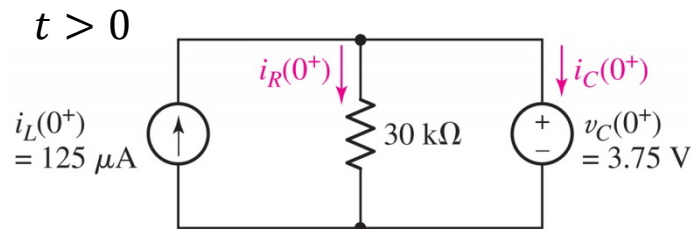
$$\therefore -3.063 \times 10^6 A_1 - 13.60 \times 10^6 A_2 = 0$$




$$i_R(t) = \begin{cases} 125 \times 10^{-6} \text{ A}, & t < 0 \\ 161.3 \times 10^{-6} e^{-3.063 \times 10^6 t} - 36.34 \times 10^{-6} e^{-13.6 \times 10^6 t} \text{ A}, & t > 0 \end{cases}$$

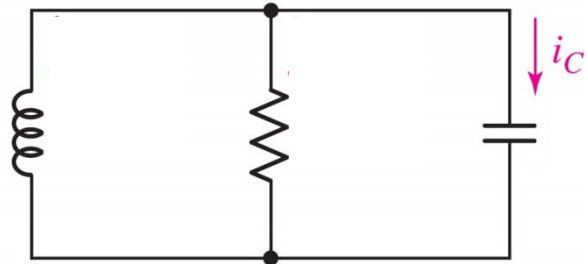Example 9.4 For $t > 0$, $i_C(t) = 2e^{-2t} - 4e^{-t}$ A. Sketch the current $0 < t < 5$ s and find settling time.


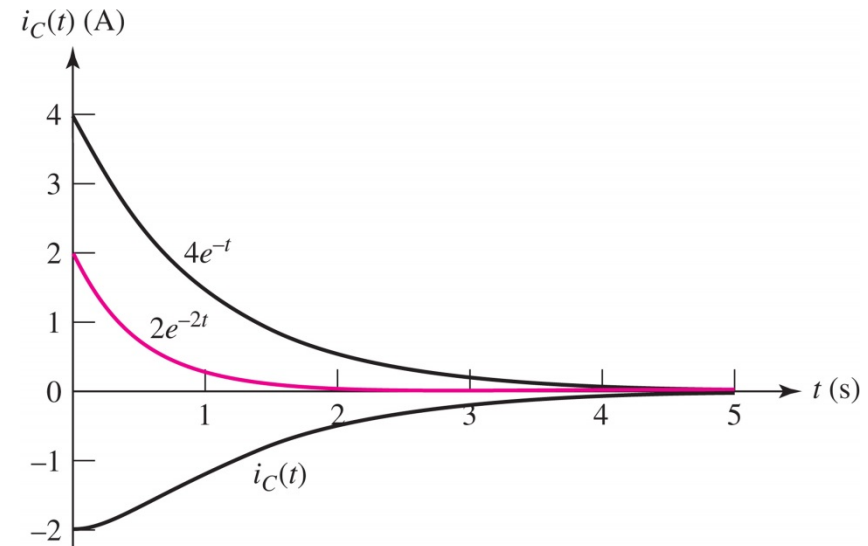
$$i_C(t) = 2e^{-2t} - 4e^{-t} \text{ A}$$




Maximum current: $i_C(t_m = 0) = -2 \text{ A}$

Settling time : 10% of maximum value.

$$i_C(t_s) = 2e^{-2t_s} - 4e^{-t_s} = -0.02$$

$$t_s = 5.296 \text{ s}$$
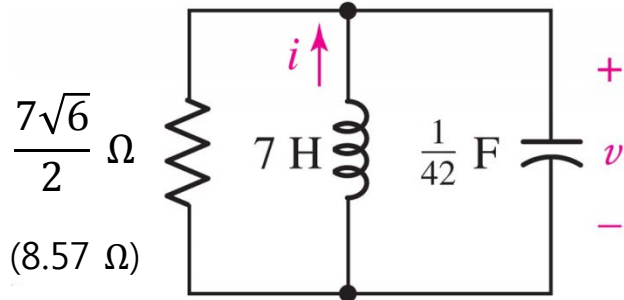
$$v(0) = 0 \text{ V}, i(0) = 10 \text{ A}$$



$$\alpha = \frac{1}{2 \frac{7\sqrt{6}}{2} \frac{1}{42}} = \frac{1}{\sqrt{7 \frac{1}{42}}} = \sqrt{6}$$

$$\omega_0 = \frac{1}{\sqrt{7 \frac{1}{42}}} = \sqrt{6}$$

$$s_1 = s_2 = -\alpha = -\sqrt{6} \text{ s}^{-1}$$

$$v(t) = ?$$

$$v(t) = A_1 e^{-\sqrt{6}t} + A_2 e^{-\sqrt{6}t} ?$$

$$v(t) = A_1 t e^{-\alpha t} + A_2 e^{-\alpha t} \\ = A_1 t e^{-\sqrt{6}t} + A_2 e^{-\sqrt{6}t}$$


$$v(0) = 0 + A_2 = 0 \rightarrow A_2 = 0$$

$$\left. \frac{dv}{dt} \right|_{t=0} = -\sqrt{6} A_1 t e^{-\sqrt{6}t} + A_1 e^{-\sqrt{6}t} = A_1$$


$$i_C = C \frac{dv_C}{dt} \rightarrow \left. \frac{dv_C}{dt} \right|_{t=0} \\ = \frac{i_C(0)}{C} = \frac{i_R(0) + i(0)}{C} = \frac{10}{\frac{1}{42}} = A_1$$

$$\therefore A_1 = 420$$

$$v(t) = 420 t e^{-\sqrt{6}t} \text{ V}$$

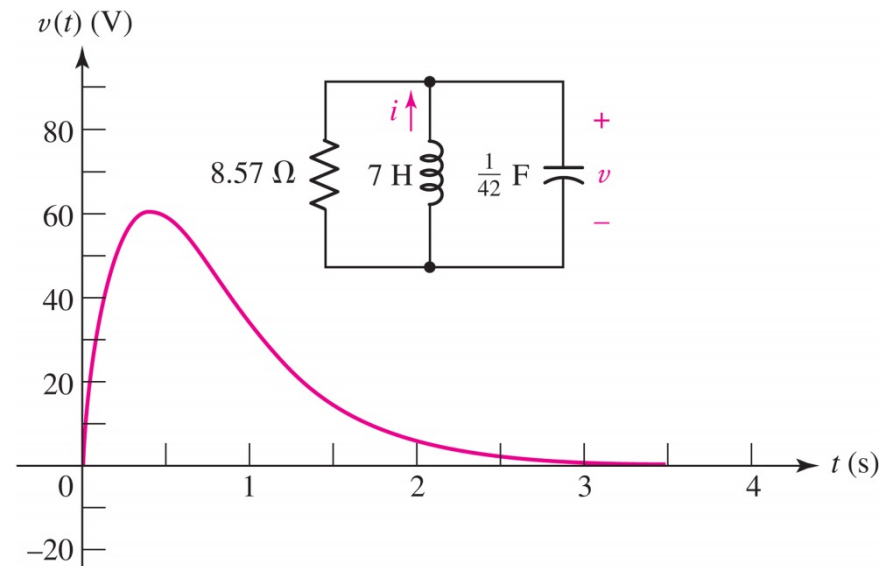

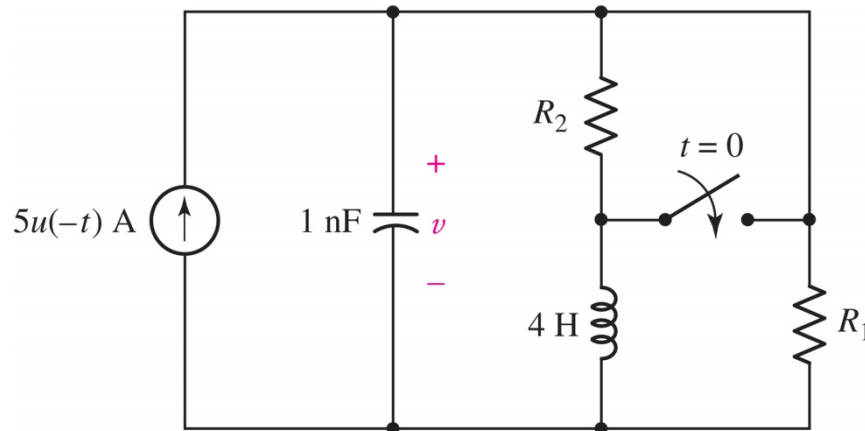Example 9.5 Find R_1 such that the circuit is critically damped for $t > 0$ and R_2 so that $v(0) = 2V$



At $t = 0^-$

$$v(0^-) = 5(R_1 \parallel R_2) = 2$$

$$\rightarrow (R_1 \parallel R_2) = \frac{2}{5} = 0.4 \Omega$$

At $t > 0$: source off, R_2 is shorted


$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 10^{-9} R_1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4 \times 10^{-9}}} = 15,810 \text{ rad/s}$$

For critical damping case

$$\alpha = \omega_0$$
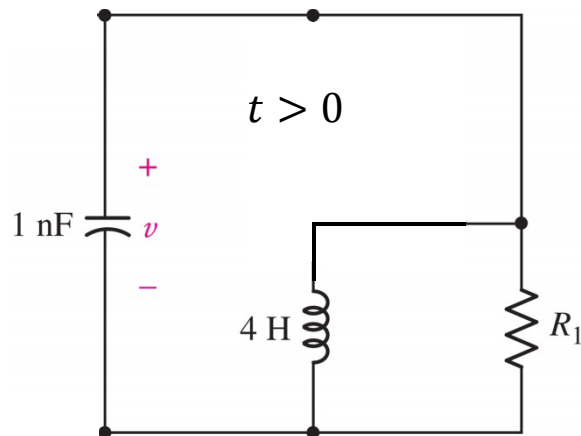
$$\rightarrow R_1 = \frac{1}{2 \times 10^{-9} \times 15810} = 31.63 \text{ k}\Omega$$



$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


$$\alpha < \omega_0 \quad \sqrt{\alpha^2 - \omega_0^2} = \sqrt{-1} \sqrt{\omega_0^2 - \alpha^2} = j \sqrt{\omega_0^2 - \alpha^2} = j\omega_d \quad \text{imaginary}$$

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} = A_1 e^{-\alpha + j\omega_d t} + A_2 e^{-\alpha - j\omega_d t} = e^{-\alpha} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t})$$

$$v(t) = e^{-\alpha} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t}) = e^{-\alpha} [A_1 (\cos \omega_d t + j \sin \omega_d t) + A_2 (\cos \omega_d t - j \sin \omega_d t)]$$

$$= e^{-\alpha} [(A_1 + A_2) \cos \omega_d t + j(A_1 - A_2) \sin \omega_d t] = e^{-\alpha} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$
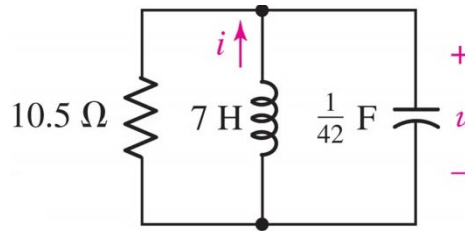
$$v(0) = 0 \text{ V}, i(0) = 10 \text{ A}$$



$$\alpha = \frac{1}{2 \times 10.5 \times \frac{1}{42}} = 2 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{7 \times \frac{1}{42}}} = \sqrt{6} \text{ rad/s}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{2} \text{ rad/s}$$

$$v(t) = e^{-2t} (B_1 \cos \sqrt{2}t + B_2 \sin \sqrt{2}t)$$

$$v(0) = B_1 = 0 \quad \rightarrow \quad v(t) = e^{-2t} B_2 \sin \sqrt{2}t$$

$$i_C = C \frac{dv}{dt} \rightarrow \left. \frac{dv}{dt} \right|_{t=0} = \sqrt{2} B_2 e^{-2t} \cos \sqrt{2}t - 2B_2 e^{-2t} \sin \sqrt{2}t \Big|_{t=0} = \sqrt{2} B_2 = \frac{i(0)}{C} = \frac{10}{\frac{1}{42}} = 420$$

$$\therefore B_2 = 210\sqrt{2}$$

$$\rightarrow v(t) = 210\sqrt{2} e^{-2t} \sin \sqrt{2}t$$


Graphical Representation of Critically Damped Response

$$v(t) = 210\sqrt{2}e^{-2t} \sin \sqrt{2}t$$


decreasing nature oscillating nature

$$\sqrt{2}t = n\pi \rightarrow v(t) = 0,$$
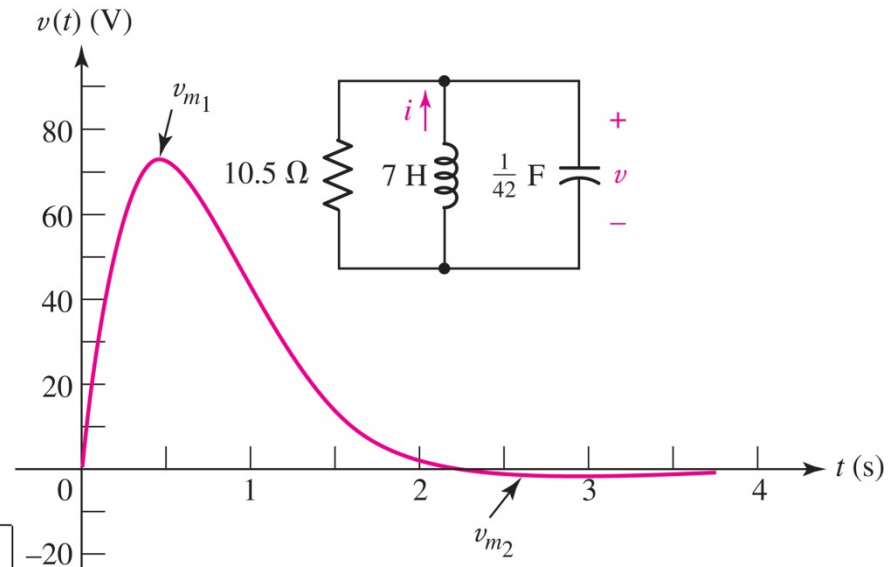
$$t = \frac{n\pi}{\sqrt{2}} \rightarrow v(t) = 0 \quad \text{Damping Oscillation!!}$$



The Role of Finite Resistance

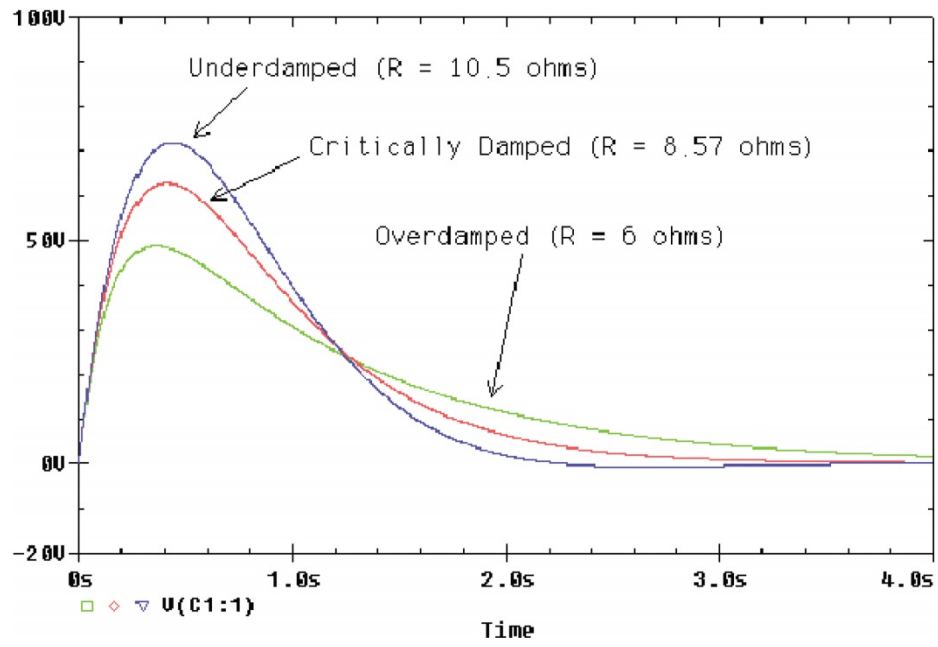

9.4 The Underdamped Parallel RLC Circuit

Example 9.6 Determine $i_L(t)$ and plot the waveform

$$\alpha = \frac{1}{2RC} = 1.2 \text{ s}^{-1} \quad \omega_0 = \frac{1}{\sqrt{LC}} = 4.899 \text{ rad/s}$$

$\alpha < \omega_0 \rightarrow$ underdamped

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 4.750 \text{ rad/s}$$

$$i_L(t) = e^{-1.2t}(B_1 \cos 4.75t + B_2 \sin 4.75t) \quad t > 0$$




$$i_L(0^-) = \frac{100}{48 + 100} 3 = 2.027 \text{ A}$$

$$v_C(0^-) = (48 \parallel 100) \times 3 = \frac{48 \times 100}{48 + 100} 3 = 97.297 \text{ V}$$

$$i_L(0^-) = i_L(0^+) = B_1 = 2.027 \text{ A}$$

$$v_C(0^+) = L \frac{di_L(0^+)}{dt} = 10 \frac{di_L(0^+)}{dt}$$
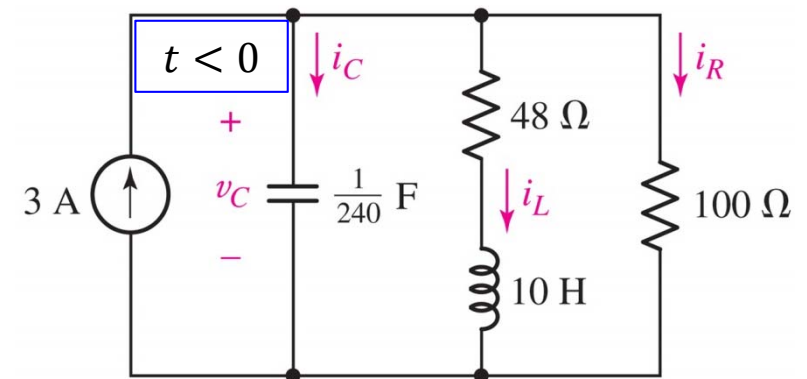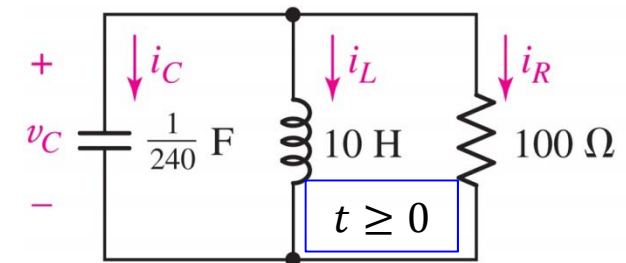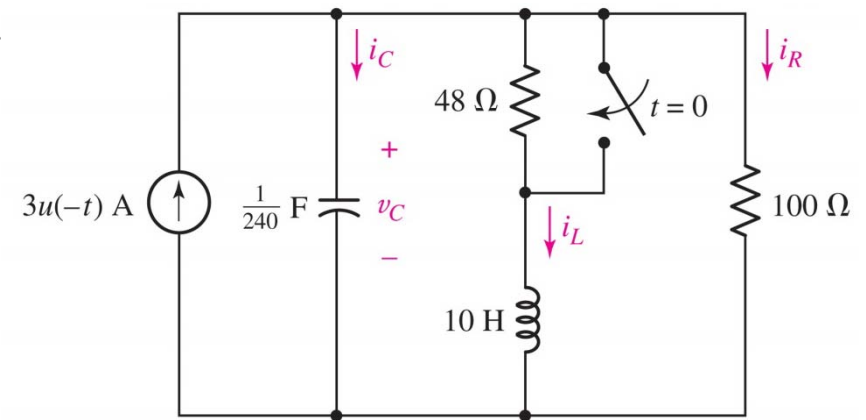
$$\rightarrow \frac{di_L(0^+)}{dt} = \frac{v_C(0^+)}{10} = \frac{v_C(0^-)}{10} = \frac{97.297}{10} = 9.73$$



9.4 The Underdamped Parallel RLC Circuit


$$i_L(t) = e^{-1.2t}(B_1 \cos 4.75t + B_2 \sin 4.75t) \quad t > 0$$


$$\frac{di_L}{dt} = e^{-1.2t}(-4.75B_1 \sin 4.75t + 4.75B_2 \cos 4.75t) - 1.2e^{-1.2t}(B_1 \cos 4.75t + B_2 \sin 4.75t)$$

$$\left. \frac{di_L}{dt} \right|_{t=0} = 4.75B_2 - 1.2B_1 = 4.75B_2 - 1.2 \times 2.027 = 9.73$$

$$\Rightarrow B_2 = \frac{9.73 + 1.2 \times 2.027}{4.75} = 2.5605$$
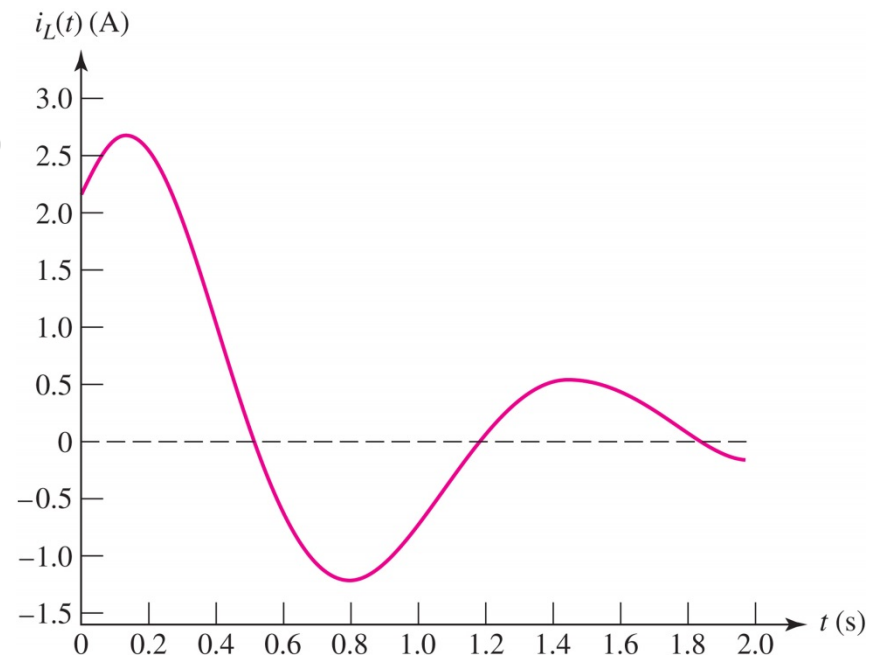
$$i_L(t) = e^{-1.2t}(2.027 \cos 4.75t + 2.5605 \sin 4.75t)$$




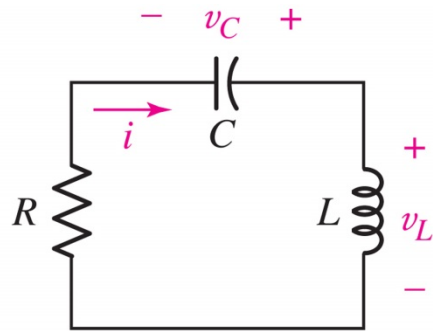

Series RLC Circuit

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int_{t_0}^t idi' - v_C(t_0) = 0$$
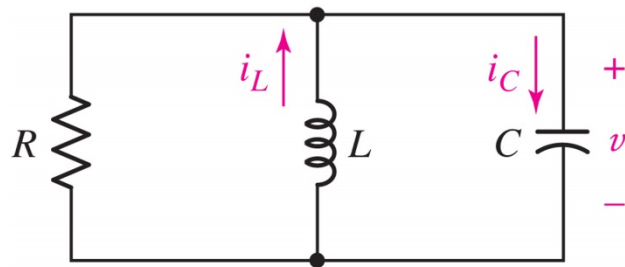
$$\rightarrow L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{1}{C}i = 0$$



Parallel RLC Circuit

$$\frac{v}{R} + \frac{1}{L} \int_{t_0}^t v dt' - i(t_0) + C \frac{dv}{dt} = 0$$

$$\rightarrow C \frac{d^2v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L}v = 0$$


Let $i(t) = Ae^{st}$ $LA s^2 e^{st} + RA s e^{st} + \frac{1}{C} A e^{st} = 0$ $\rightarrow Ae^{st} \left(Ls^2 + Rs + \frac{1}{C} \right) = 0$

$$s_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad s_2 = -\frac{R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad \alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

TABLE 9.1 Summary of Relevant Equations for Source-Free *RLC* Circuits

Type	Condition	Criteria	α	ω_0	Response
Parallel Series	Overdamped	$\alpha > \omega_0$	$\frac{1}{2RC}$ $\frac{R}{2L}$	$\frac{1}{\sqrt{LC}}$	$A_1 e^{s_1 t} + A_2 e^{s_2 t}$, where $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega^2}$
Parallel Series	Critically damped	$\alpha = \omega_0$	$\frac{1}{2RC}$ $\frac{R}{2L}$	$\frac{1}{\sqrt{LC}}$	$e^{-\alpha t} (A_1 t + A_2)$
Parallel Series	Underdamped	$\alpha < \omega_0$	$\frac{1}{2RC}$ $\frac{R}{2L}$	$\frac{1}{\sqrt{LC}}$	$e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$, where $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$

Example 9.7 Determine $i(t)$

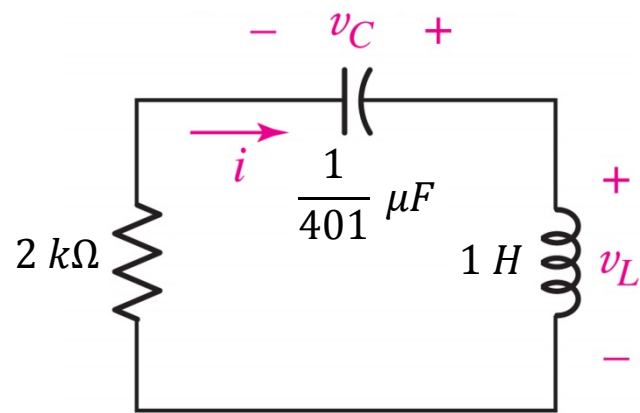

$$i(0) = 2 \text{ mA}, \quad v_C(0) = 2 \text{ V} \quad \alpha < \omega_0 \rightarrow \text{underdamped}$$

$$\alpha = \frac{R}{2L} = 1000 \text{ s}^{-1} \quad \omega_0 = \frac{1}{\sqrt{1 \times \frac{1}{401} \times 10^{-6}}} = 20025 \text{ rad/s}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 20000 \text{ rad/s}$$

$$i(t) = e^{-1000t} (B_1 \cos 20000t + B_2 \sin 20000t) \quad \rightarrow \quad i(0) = B_1 = 2 \times 10^{-3} \text{ A}$$


$$L \frac{di}{dt} + Ri - v_C = 0 \rightarrow \frac{di}{dt} = \frac{v_C - 2000i}{L}$$

$$\Rightarrow \left. \frac{di}{dt} \right|_{t=0} = \frac{v_C(0) - 2000 \times i(0)}{1} = -2$$


$$\left. \frac{di_L}{dt} \right|_{t=0} = 20000B_2 - 1000 \times B_1$$

$$= 20000B_2 - 2 = -2 \Rightarrow B_2 = \frac{0}{20000} = 0$$

$$i(t) = 2 \times 10^{-3} e^{-1000t} \cos 20000t \text{ A } t > 0$$

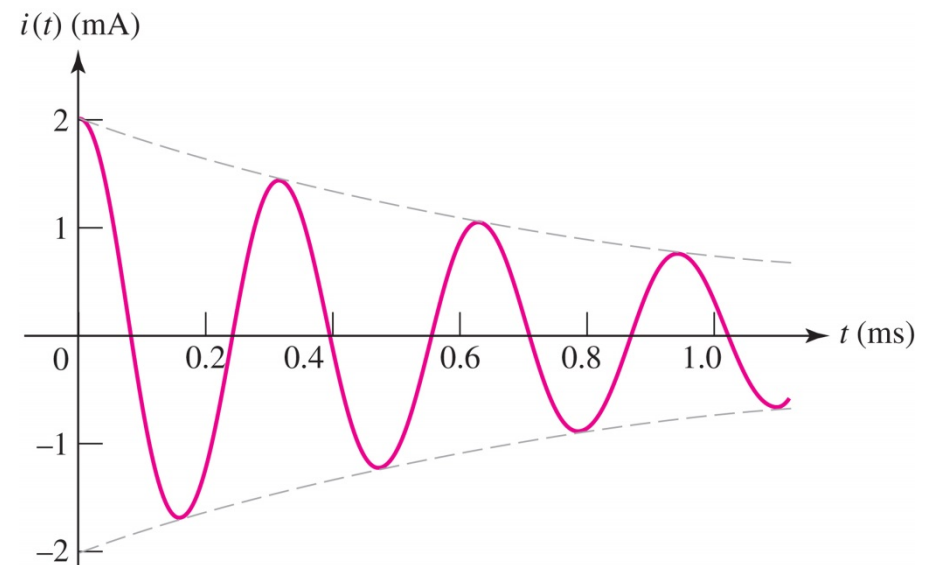

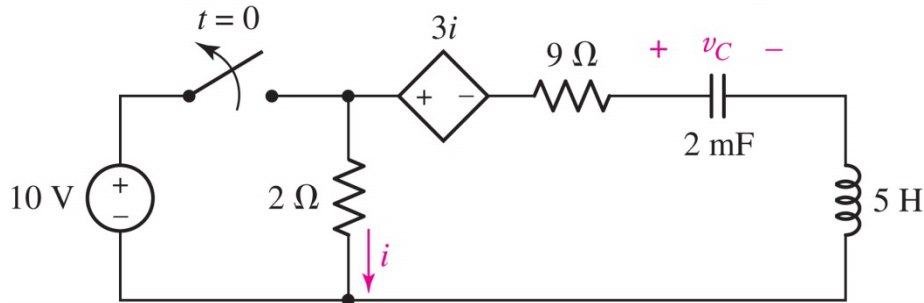Example 9.8 Determine $v_C(t)$ for $t > 0$.




At $t = 0^-$

$$i_L(0^-) = 0 \text{ A},$$

$$i(0^-) = \frac{10}{2} = 5 \text{ A},$$

$$10 = 3i(0^-) + v_C(0^-)$$
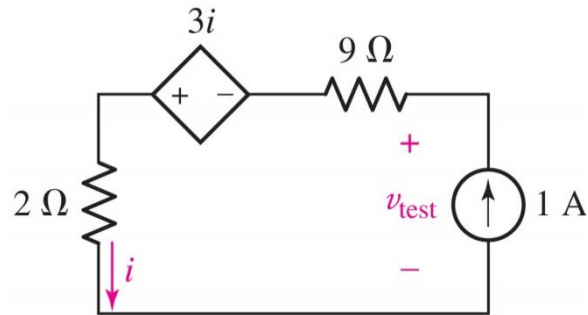
$$\rightarrow v_C(0^-) = 10 - 3 \times 5 = -5 \text{ V}$$



$$R_{eq} = \frac{v_{test}}{1 \text{ A}} = \frac{11 \times 1 - 3i}{1 \text{ A}} = 8 \Omega$$

$$L = 5, \\ C = 2 \times 10^{-3},$$

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0 \Rightarrow 5 \frac{d^2 i}{dt^2} + 8 \frac{di}{dt} + \frac{1}{2 \times 10^{-3}} i = 0$$

$$\alpha = \frac{R}{2L} = \frac{8}{2 \times 5} = 0.8 \text{ s}^{-1},$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{5 \times 2 \times 10^{-3}}} = 10 \text{ rad/s}$$

$\alpha < \omega_0 \rightarrow$ underdamped

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 9.968 \text{ rad/s}$$

$$v_C(t) = e^{-0.8t} (B_1 \cos 9.968t + B_2 \sin 9.968t)$$


$$v_C(0^-) = v_C(0^+) = B_1 = -5 \text{ V}$$

$$i = -C \frac{dv_C}{dt} \rightarrow \frac{dv_C}{dt} = -\frac{i}{C} \Rightarrow \left. \frac{dv_C}{dt} \right|_{t=0} = -\frac{i(0^+)}{C} \\ = -\frac{i_L(0^-)}{C} = -\frac{0}{2 \times 10^{-3}} = 0$$

$$\frac{dv_C}{dt} = e^{-0.8t}(-9.968B_1 \sin 9.968t + 9.968B_2 \cos 9.968t) - 0.8e^{-0.8t}(B_1 \cos 9.968t + B_2 \sin 9.968t)$$

$$\left. \frac{dv_C}{dt} \right|_{t=0} = 9.968B_2 - 0.8 \times B_1 = 9.968B_2 + 4 = 0 \quad \Rightarrow \quad B_2 = \frac{-4}{9.968} = -0.4013 \text{ V}$$
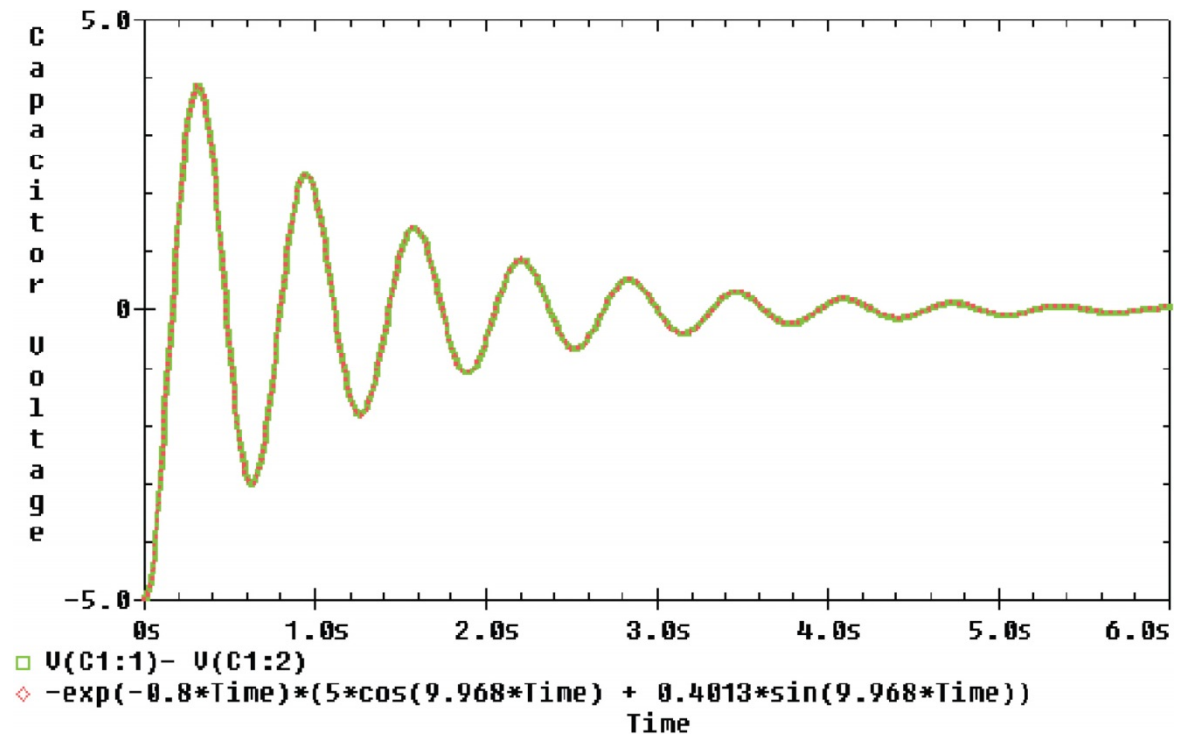
$$v_C(t) = -e^{-0.8t}(5 \cos 9.968t + 0.4013 \sin 9.968t)$$



- General Solution

1. Determine the **initial conditions**.
2. Obtain a numerical value for the **forced response**.
3. Write the appropriate form of the **natural response** with the necessary number of arbitrary constants.
4. **Add the forced response and natural response** to form the complete response.
5. **Evaluate** the response and its derivative at $t = 0$, and employ the initial conditions to solve for the values of the unknown constants.

Forced response $v_f(t) = V_f$

Natural response $v_n(t) = Ae^{s_1t} + Be^{s_2t}$

$$v_n(t) = e^{-\alpha}(B_1 \cos \omega_d + B_2 \sin \omega_d)$$



$$v_n(t) = A_1te^{-\alpha t} + A_2e^{-\alpha t}$$

$$\Rightarrow v(t) = V_f + Ae^{s_1t} + Be^{s_2t}$$

$$\frac{dv}{dt} = 0 + s_1Ae^{s_1t} + s_2Be^{s_2t}$$

9.6 The Complete Response of the *RLC* Circuit

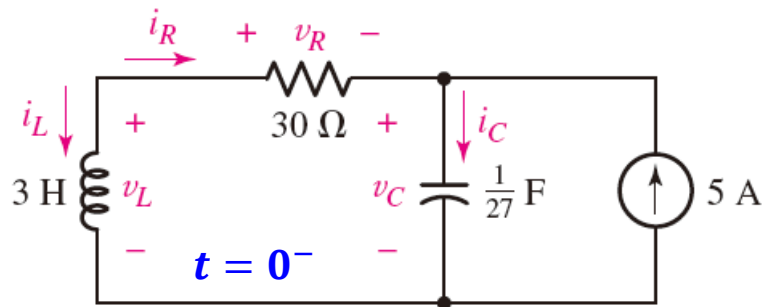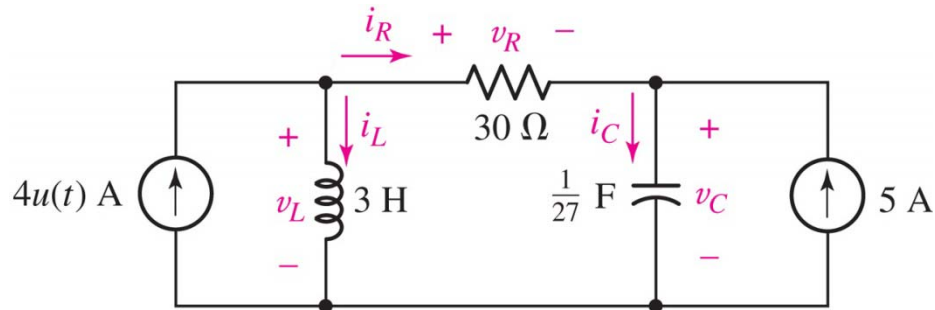Example 9.9 Find the values of these six quantities at both $t=0^-$ and $t=0^+$.




$$v_L(0^-) = 0, \quad i_C(0^-) = 0 \text{ for dc current source}$$

$$i_R(0^-) = -5 \text{ A}, \quad v_R(0^-) = 30 \times (-5) = -150 \text{ V},$$

$$v_C(0^-) = -v_R(0^-) = 150 \text{ V},$$

$$i_L(0^-) = -i_R(0^-) = 5 \text{ A}$$

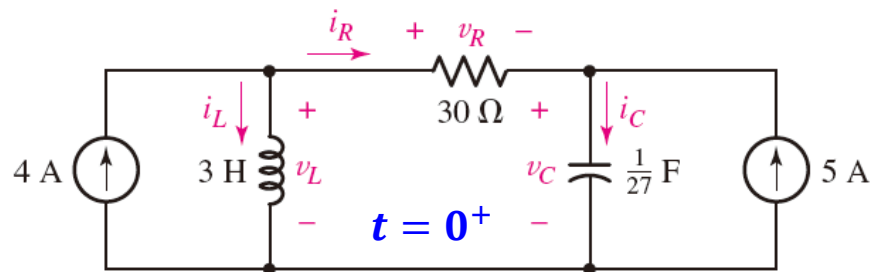

$$i_L(0^+) = i_L(0^-) = 5 \text{ A}, \quad v_C(0^+) = v_C(0^-) = 150 \text{ V}$$


$$i_R(0^+) = 4 - i_L(0^+) = 4 - 5 = -1 \text{ A},$$

$$v_R(0^+) = 30 \times i_R(0^+) = 30 \times (-1) = -30 \text{ V},$$

$$i_C(0^+) = 5 + i_R(0^+) = 5 - 1 = 4 \text{ A},$$

$$v_L(0^+) = v_R(0^+) + v_C(0^+) = -30 + 150 = 120 \text{ V}$$

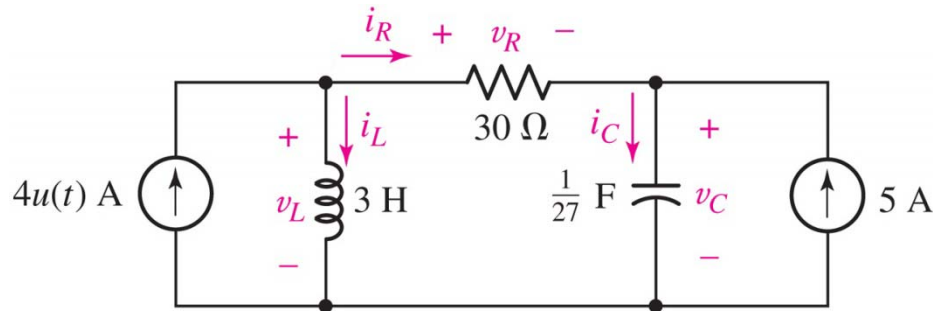Example 9.10 Find the determination of the initial conditions



$$v_L = L \frac{di_L}{dt} \rightarrow \left. \frac{di_L}{dt} \right|_{t=0^+} = \frac{v_L(0^+)}{L} = \frac{120}{3} = 40,$$

$$i_C = C \frac{dv_C}{dt} \rightarrow \left. \frac{dv_C}{dt} \right|_{t=0^+} = \frac{i_C(0^+)}{C} = \frac{4}{1/27} = 108,$$


$$i_R = 4 - i_L \rightarrow \left. \frac{di_R}{dt} \right|_{t=0^+} = -\left. \frac{di_L}{dt} \right|_{t=0^+} = -40,$$

$$v_R = 30 \times i_R \rightarrow \left. \frac{dv_R}{dt} \right|_{t=0^+} = 30 \left. \frac{di_R}{dt} \right|_{t=0^+} = -1200,$$

$$v_L = v_R + v_C \rightarrow \left. \frac{dv_L}{dt} \right|_{t=0^+} = \left. \frac{dv_R}{dt} \right|_{t=0^+} + \left. \frac{dv_C}{dt} \right|_{t=0^+} = -1200 + 108 = -1092,$$

$$i_C = 5 - (-i_R) \rightarrow \left. \frac{di_C}{dt} \right|_{t=0^+} = \left. \frac{di_R}{dt} \right|_{t=0^+} = -40$$

Find $v_C(t)$ for $t > 0$.

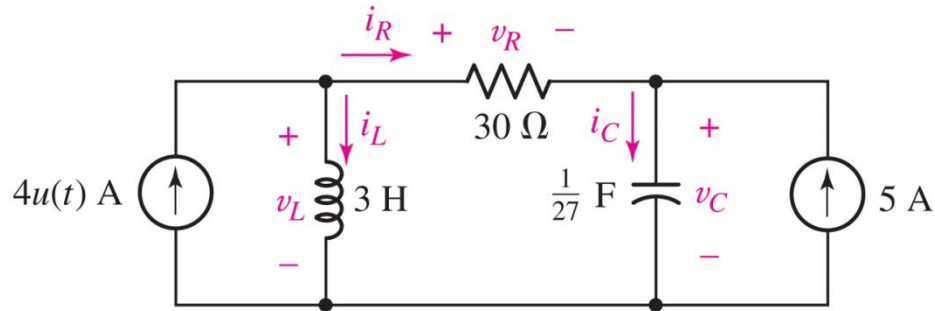

Forced response

$$v_{C_f}(t) = v_C(\infty) = 150 \text{ V}$$

Complete response

$$v_C(t) = 150 + Ae^{-t} + Be^{-9t}$$

$$v_C(0^+) = 150 + A + B = 150$$

$$\rightarrow A + B = 0$$

$$A = 13.5, \quad B = -13.5$$

$$\alpha = \frac{R}{2L} = \frac{30}{2 \times 3} = 5 \text{ s}^{-1},$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{3 \times \frac{1}{27}}} = 3 \text{ rad/s}$$

$$\alpha > \omega_0 \rightarrow \text{overdamped}$$

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -5 \pm 4$$


$$\rightarrow s_1 = -1, s_2 = -9$$

$$\frac{dv_C}{dt} = -Ae^{-t} - 9Be^{-9t} = \frac{i_C(t)}{C}$$

$$\Rightarrow \left. \frac{dv_C}{dt} \right|_{t=0^+} = -A - 9B = \frac{4}{\frac{1}{27}} = 108$$

$$v_C(t) = 150 + 13.5(e^{-t} - Be^{-9t}) \quad t > 0$$

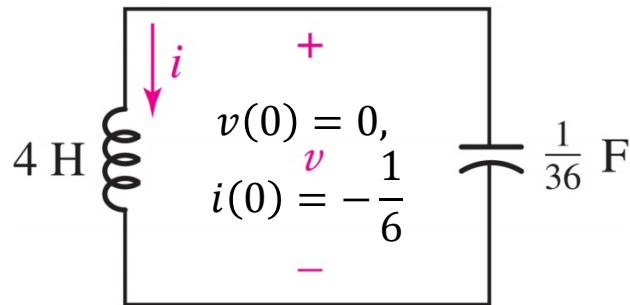- The resistor in the RLC circuit serves to dissipate initial stored energy.
- When this resistor becomes 0 in the series RLC or infinite in the parallel RLC, the circuit will oscillate.



$$\alpha = \frac{R}{2L} = 0 \text{ s}^{-1}, \quad \omega_0 = \frac{1}{\sqrt{4 \times \frac{1}{36}}} = 3 \text{ rad/s}$$

$$\alpha < \omega_0 \rightarrow \text{underdamped}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 3$$

$$v = A \cos 3t + B \sin 3t,$$

$$v(0) = A = 0$$

$$\frac{dv}{dt} = 3B \cos 3t \rightarrow \frac{dv}{dt} \Big|_{t=0} = 3B = 6$$

$$\Rightarrow B = 2$$

$$i = -C \frac{dv}{dt} \rightarrow \frac{dv}{dt} \Big|_{t=0} = -\frac{i(0)}{C} = -\frac{-\frac{1}{6}}{\frac{1}{36}} = 6$$

$$v(t) = 2 \sin 3t \quad t > 0 \quad \text{Does not decay}$$

$$\frac{1}{4} \int_0^t v dt' - i(0) + \frac{1}{36} \frac{dv}{dt} = 0 \rightarrow \frac{1}{4} v + \frac{1}{36} \frac{d^2v}{dt^2} = 0 \Rightarrow \frac{d^2v}{dt^2} + 9v = 0 \Rightarrow v(t) = \sin 3t$$

General solution

이 자료에 나오는 모든 그림은 McGraw-hill 출판사로부터 제공받은 그림을 사용하였음.

All figures at this slide file are provided from The McGraw-hill company.